

GANPAT UNIVERSITY
B.TECH SEM.1st (ME/MC/Civil/EE)
REGULAR EXAMINATION NOV-DEC 2012
EE101: ELEMENTS OF ELECTRICAL ENGINEERING

TIME:-3 HOURS

TOTAL MARKS-70


- INSTRUCTION:-**
1. Attempt all questions.
 2. Make suitable assumptions wherever necessary.
 3. Figures to the right indicate full marks.

Section-I

- Que-1**
- (a) Derive the conditions for maximum power transfer when load consists of a variable resistance for D.C (04)
 - (b) Derive an expression for the capacitance of a parallel plate with composite medium. (04)
 - (c) Derive expressions of equivalent inductance when two magnetically coupled coils are connected in parallel in two different ways. (04)

OR

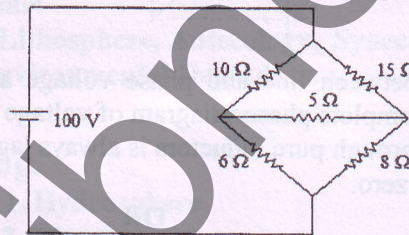- Que-1**
- (a) Explain the method of transforming a star network of resistances into delta network. (04)
 - (b) Derive equation for charging of capacitor in RC circuit. Also define time constant of circuit. (04)
 - (c) Using thevenin's theorem, find the current in 5Ω resistor in the circuit as shown in below figure. (04)



- Que-2**
- (a) Explain Joule's law of electric heating. (03)
 - (b) Derive the equation of co-efficient of coupling. (04)
 - (c) A coil is wound uniformly with 300 turns over a steel ring of relative permeability 900 having a mean diameter of 20 cm. The steel ring is made of a bar having cross section of diameter 2cm. If the coil has resistance of 50Ω and is connect to 250 V DC supply. Calculate the (i) mmf (ii) field intensity of the ring (iii)reluctance (iv)total flux (v) permeance (04)

OR

- Que-2**
- (a) Explain lead-acid Battery. (03)
 - (b) Explain self inductance and derive the methods for finding self inductance. (04)
 - (c) A capacitor is charged to a d.c source a resistor of $1M\Omega$. If in 1 second, the potential difference across the capacitor reaches 80 % of the final value, calculate the capacitance of the capacitor. (04)

- Que-3** **Attempt Any Three** (12)
- (a) Define (i) Leakage co-efficient (ii) Reluctance (iii) Magnetic fringing.
 - (b) Explain the laws of illumination.
 - (c) Bring out the analogy between electric and magnetic circuit.
 - (d) Explain multi plate capacitor.


Section-II

- Que-4** (a) Explain following terms: (i) Frequency (ii) Crest factor (iii) Average Value (iv) Phase difference (04)
- (b) Obtain RMS value for sinusoidal alternating current and half wave rectified output waveform. (04)
- (c) Find the circuit constants of a two element series circuit which consumes 700 W with a power of 0.707 leading. The applied voltage is $V=141.4\sin 314t$. (04)

OR

- Que-4** (a) State the condition for series R-L-C resonance circuit. Derive the equation for resonant frequency and Q-factor. (04)
- (b) What do you mean by admittance of a circuit? And draw admittance triangle of RL and RC series circuit. (04)
- (c) The Circuit having Two Impedances of $Z_1=8+j15 \Omega$ and $Z_2=6-j8 \Omega$ in Parallel, is Connected to A Single Phase Ac Supply And The Current Drawn is 10A. Find Each Branch Current, Both in Magnitude and Phase, and also the Supply Voltage (04)

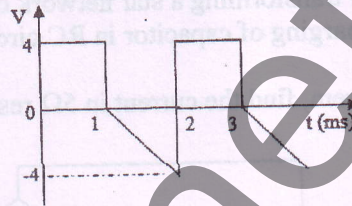- Que-5** (a) Calculate the r.m.s. value of the voltage waveform shown in below Fig. (03)



- (b) Establish relation between line and phase voltage and current in balanced delta connection. Draw complete phasor diagram of voltage and currents. (04)
- (c) Prove that current through pure inductors is always lagging by 90° to its voltage and power consumed is zero. (04)

OR

- Que-5** (a) A balanced 3-phase star connected load of 120 KW takes a leading current of 100 A when connected across 3-phase, 3.3 KV, 50 Hz supply. Determine the impedance, resistance, and power factor of the load. (03)
- (b) Explain Two Wattmeter method for measurement of 3- ϕ power. (04)
- (c) Define following terms: (i) Load Curve, (ii) Load Factor, (iii) Demand Factor, (iv) Connected Load (04)

Que-6 Attempt Any Three (12)

- (a) Discuss Tariff and its types.
- (b) Discuss construction and application of ELCB
- (c) Write a short note on PMMC.
- (d) Explain parallel resonance.

-----END OF PAPER-----