Exam No: _

Evming 12/2015

GANPAT UNIVERSITY

B. TECHSEM (ALL BRANCHES) RECULAR/REMEDIAL (CBCS NEW) EXAMINATION- NOV-DEC 2015 2EE101: ELEMENTS OF ELECTRICAL ENGINEERING

TIME: 3 HRS

TOTAL MARKS: 60

Instructions: (1) This Question paper has two sections. Attempt each section in separate answer book.

- (2) Figures on right indicate marks.
- (3) Be precise and to the point in answering the descriptive questions
- (4) Assume suitable data whenever required.

SECTION: I

Q.1	[A [B	 Discuss Permittivity, Electrical Potential and Electric field strength. Derive expression for the capacitance of a parallel plate capacitor with uniform dielectric medium. 	[3] [4]
	[C	Define Time constant and explain in detail.	[3]
0.1		OR	
Q.1	[A]	A capacitor is charged through a resistance of $500k\Omega$ connected in series with it across a dc supply. The potential difference across the capacitor is 80% of its final value after 1	[5]
	(D)	second during charging. Find the value of the capacitance.	
	נסן	Permeability.	[5]
Q.2	[A]	Compare magnetic circuit with electric circuit.	[5]
	[B]	What is the co efficient of coupling? Derive an expression for the same.	[5]
		OR	[-]
Q.2	[A]	Two coils are connected in series and derive the expression for net inductance of the coil in i) series aiding connection and ii) series opposing connection.	[5]
	[B]	A coil is wound uniformly with 300 turns over a steel ring of relative permeability 900 having a mean diameter of 20cm and flux of 3mwb. The steel ring is made of bar a	[5]
		having cross section of diameter 2cm. Find mmf. Neglect magnetic leakage.	
Q.3	Atte	mpt the following questions	
	[A]	Explain joule's law of electric heating and discuss thermal efficiency	[03]
	[B]	Describe in brief the requirements of good lighting	[03]
	[C]	Discuss self inductance.	[02]
	[D]	The total inductance of two coils, A and B when connected in series is 0.5H or 0.2H, depending on the relative directions of the current in coils. Coil A, when isolated from	[03]
		coil B has a self inductance 0.2 H. Calculate (1) The mutual inductance between two coils, (2) The self inductance of coil B, (3) Coupling factor between two coils	

SECTION: II

- Q.4 [A] Derive the equation of transforming star connected network into delta connected [5] network and vice versa.
 - [B] Fig. shows a circuit feeding a load Resistance R_L (1) Find the value of R_L so that it [5] draws maximum power. Calculate this power. (2) When R_L is adjusted for maximum power transfer, what percentage of power delivered by the battery reaches R_L?



OR

[2]

[5]

[3]

[2]

[4]

[3]

[03]

- Q.4 [A] Discuss Laws of Resistance.
 - [B] Compare Series resistance with parallel resistance.
 - [C] State Superposition theorem and explain with necessary diagram and equation.
- Q.5 [A] Define Time period and Peak factor.
 - [B] Explain phasor methods to solve parallel circuit with necessary diagram.
 - [C] State the condition for parallel resonance and obtain equation for resonant frequency. [4]

OR

- Q.5 [A] Draw circuit diagram, phasor diagram and wave diagram for series R-L circuit.
 - [B] Obtain r.m.s value, average value, form factor and peak factor for full wave rectified [4] circuit.
 - [C] A non-inductive resistance of 10 Ω is connected in series with an inductive coil across [3] 200V, 50Hz ac supply. The current drawn by the series combination is 10A. The resistance of the coil is 2 Ω. Determine (1) Inductance of the coil (2) Power Factor (3) Voltage across the coil.

Q.6 Attempt the following questions.

- [A] Explain Two wattmeter method for measurement of 3-phase power and prove that [03] $W_1+W_2 = \sqrt{3} V_L I_L \cos \varphi$.
- [B] A balanced 3-phase star connected load of 18kw takes a leading current of 60A when [02] connected across 3-phase, 440V, 50 Hz supply. Determine impedance, resistance, and capacitance and power factor of the load.
- [C] What do you mean by tariff? And Discuss important types of tariff.
- [D] An impedance of $(7+j5)\Omega$ is connected in parallel with another circuit having an [02] impedance of $(10-j8)\Omega$. The supply voltage is 230V, 50Hz. Calculate (1) the admittance, conductance and susceptance of the circuit, (2) the total current and (3) power factor.

END OF PAPER---

ALL THE BEST