Student Exam No:-\_

Total Marks:-70

## GANPAT UNIVERSITY B.TECH SEM-II (CE/IT/EC/BM &I) MARINE) REGULAR EXAMINATION MAY-2014 2EE101:-ELEMENTS OF ELECTRICAL ENGINEERING

Time: 3 Hours

Qı

Qu

Jue

Instructions: - 1. Attempt all questions.

- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

## SECTION-I

Q:1	(A)	Discuss leakage flux and leakage co-efficient. Compare Magnetic circuit with electric	(6)
	<b>(B)</b>	Derive the equation for the total inductance when two coils are connected in series.	(6)
0.1	(	Discuss main north of Dattery and write application of battery	(6)
Q:1	(A)	Discuss main parts of Battery and write application of battery.	(0)
	(B)	State and describe various types of lighting schemes.	(6)
Q:2	(A)	What is capacitor? why series resistance is connected during charging and discharging? Discuss multiple parallel plate capacitor.	(6)
	(B)	Define mutual inductance. Describe a method to measure the mutual inductance between the coils.	(5)
		OR	
0.2	(1)	State and evolain maximum nower transfer theorem	(6)
2.4	(A) (D)	A D C voltage V is applied across a circuit consisting of resistance R ohm in series	(5)
	(B)	with a capacitor of capacitance C farads. Derive an expression for variation of voltage	(0)
~ ~		deross capacitor with time.	(12)
Q:3		Attempt any three:	(14)
	(A)	Determine the current through the 2 onm resistor of fig. Using Norton's theorem	
		au all Stohm Z tohm	

- (B) Two 75 turns coils are wound on an iron core that has closed magnetic path. The core dimension are length of 30 cm and cross section area of  $9 \text{ cm}^2$ . If the core has relative permeability of 900, Calculate the inductance of each coil, mutual inductance and co efficient of coupling.
- (C) Two heaters A and B are in parallel across supply voltage V. Heater A produces 500 K cal in 20 minutes and B produces 1000 K cal in 10 minutes. The resistance of A is 10 ohm. Calculate the resistance of B. If the same heaters are connected in series across same voltage, how much heat will produced in 5 minutes?
  (D) Explain magnetic hysteresis.

Page 1 of 2

## SECTION-II

0.4	(1)	Discuss rms value, average value, peak factor and phase difference.	(6)
Q:4	(A) (B)	Derive the relationship between the voltage and current for a purely inductive circuit connected to ac supply .Also show that the average power consumed by circuit is zero	(6)
		OR	10
0.4	(A)	What is impedance triangle? Draw vector, phasor and impedance triangles for (i) R-L	(6)
Y.1	(1.4)	series circuit and (ii) R-C series circuit.	
	(B)	Explain Phasor method to solve parallel ac circuit.	(6)
0.5		With pagessary diagram and equation explain parallel resonance.	(6)
Q:5	(A)	with necessary diagram and equation express produce and line voltage (ii) phase current and	(5)
	(B)	What is the relation between (1) phase voltage and the voltage (1) provide the	
		line current for star connection? Derive these relations.	
		OR	(6)
0:5	(A)	Discuss fuse ,MCB and ELCB.	(0)
×	(B)	Explain Construction and working principle of PMMC.	(5)
0.6	(2)	Attempt any three:	(12)
2.0	(1)	Define Tariff and Explain different types of tariff.	
	(A)	Define faint and Explain and the measure power in a three phase circuit. The reading	
	(B)	Two wattmeter are connected to measure power factor is unity. If the power factor of	
		of the one of the meter is SK w when load power lactor is diff. If the power Calculate	
		the load is changed to 0.707 lagging without changing the total input power, calculate	

- the readings of the two wattmeter.
   (C) A resistance of 50 ohm, an inductance of 0.15 H and a capacitance of 100 μF are connected in parallel across the 100 V, 50 Hz supply. Calculate (a) the current in each branch (b) the total current (c) power factor of the circuit.
- (D) An a.c circuit consist of a pure resistance of 10 ohms and is connected across a a.c supply of 230 V, 50 Hz. Calculate (i) current (ii) power consumed and (iii) write down the equation of voltage and current.

