

GANPAT UNIVERSITY
B.TECH SEM.III BIOMEDICAL & INSTRUMENTATION ENGINEERING
REGULAR EXAMINATION NOV-DEC 2011
2BM301: LINEAR ELECTRONICS

TIME: 3 HOURS

TOTAL MARKS-70

INSTRUCTION: -1. Answers to the 2 sections must be written in the separate answer books
 2. Figures to the right indicate marks.
 3. Conventional terms or notation are used.

SECTION-I

Que.-1

12

- (a) Explain the Transistor regions. And also Explain the Voltage divider Biasing of the transistor?
- (b) Explain the BJT r_e Model for (i) CB configuration (ii) CE configuration.

OR

Que.-1

12

- (a) Write short note on BJT modeling and derive the equation of the input impedance, output impedance, voltage gain, current gain.
- (b) Explain operating Point & Load line. Derive the Equations of operating point for the Emitter stabilized Bias Configuration

Que.-2

11

- (a) Explain in brief types of power amplifier? Explain the series fed class 'A' amplifier?
- (b) For a common base configuration of fig. 1 with $I_E=4mA$, $\alpha=0.991$ & AC signal of $3mV$ applied between the base & emitter terminals;
 1. Determine the i/p impedance
 2. Calculate the voltage gain if a load of 610Ω is connected to the output terminals.
 3. Find the output impedance & current gain.

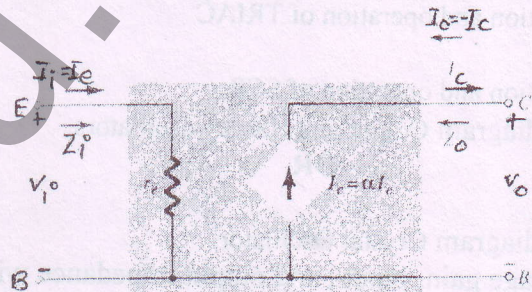


fig:1

OR

Que.-2

11

- (a) What are the Advantages of the negative feedback system & explain the effect of negative feedback on Gain & Bandwidth? And also Obtain the Voltage gain for voltage- series feedback.
- (b) Calculate the values of collector current, emitter current & β_{dc} for transistor with $\alpha_{dc}=0.99$ & $I_{CBO}=5\mu A$, $I_B=100\mu A$.

Que.-3

12

- (a) Explain the BJT two ports Model with its parameters.
- (b) Explain the Darlington pair connection in brief
- (c) Explain the transformer coupled Class 'B' amplifier.
- (d) Draw the d.c. load line for the emitter circuit when $V_{cc}=16V$, $R_c=2K\Omega$, $V_{BB}=16V$, $R_B=100K\Omega$ & $h_{fe}=100$.

SECTION-II

Que.-4

12

- (a) Explain the effects of R_S & R_L on BJT.
- (b) For the network shown in fig.2 determine: i) r_e , ii) Z_i , iii) Z_o , and iv) A_v

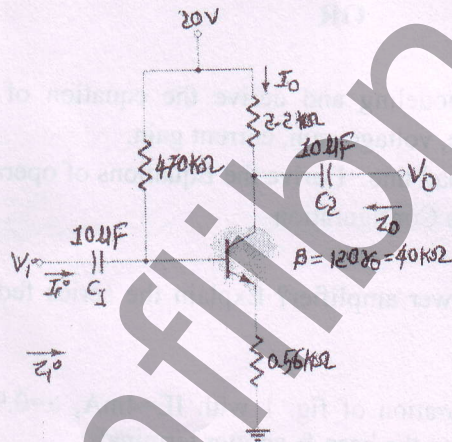


Fig.2

OR

Que.-4

12

- (a) Explain the construction and operation of n channel JFET
- (b) Explain the construction and operation of TRIAC

Que.-5

11

- (a) Explain the construction and operation of SCR
- (b) Explain with neat diagram Colpitt and Hartley oscillators.

OR

Que.-5

11

- (a) Explain with neat diagram Crystal Oscillator.
- (b) Determine the voltage gain, input, and output impedance with feedback for voltage series feedback having $A=-100$, $R_i=10K\Omega$, and $R_o=20K\Omega$ for feedback of i) $\beta=-0.1$ and ii) $\beta=-0.5$

Que.-6

Answer the following question(Any Two)

12

- (a) Describe the Basic operation of the oscillator.
- (b) Explain the Emitter follower circuit with neat diagram and derive the equation for voltage gain.
- (c) Describe with neat diagram Wein Bridge Oscillator with Lead Lag Circuit

END OF PAPER

gnu.inflibnet.ac.in