

Seat No: \_\_\_\_\_

**GANPAT UNIVERSITY**  
**B.TECH SEM. III BIOMEDICAL & INSTRUMENTATION ENGINEERING**  
**CBCS REGULAR EXAMINATION DECEMBER 2013**  
**2BM 301: LINEAR ELECTRONICS**

**TIME: - 3 HOURS** **TOTAL MARKS: - 70**  
**INSTRUCTION: -** 1. Write the answer of each section in separate answer sheet.  
2. Figure to the right indicates full marks.  
3. Assume suitable data if necessary.


**SECTION-I**

- Que-1
- (a) Define: 6  
Electronics, Amplifier, Bandwidth, Frequency response, Biasing, Oscillator
  - (b) What is biasing? Name the types of biasing. Explain any one type of it. 6

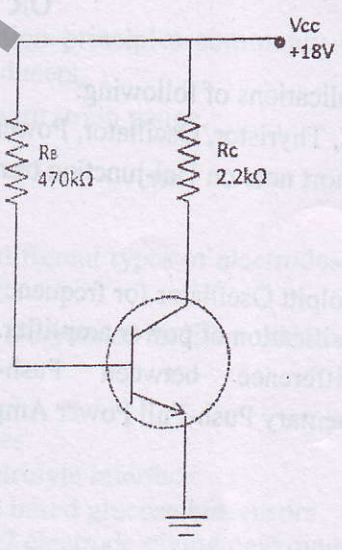**OR**

- Que-1
- (a) Explain CB characteristics of BJT with neat diagram. 6
  - (b) Draw and explain Hartley oscillator. 6

- Que-2
- (a) Compare: FET and BJT. 2
  - (b) Draw load line for fixed bias circuit showing below. 9  
For  $h_{FE} = 50, 100, 200$ . And also give your view on stability of all.





OR

- Que-2
- (a) Give the difference between Zener breakdown and Avalanche breakdown. 2
  - (b) Design amplifier for  $V_{cc} = +24V$ . The signal source resistance is  $600\Omega$  and lower cutoff frequency is to be 100Hz,  $h_{fe} = 100$  and  $h_{ie} = 1k\Omega$ . 9

- Que-3
- (a) What is feedback? What are the types of feedback? Write merits and demerits of feedback. 4
  - (b) Draw ac analysis and h-parameter model for CE amplifier with bypass capacitor. 4
  - (c) Explain Darlington pair with necessary diagrams. 4

SECTION-II

- Que-4
- (a) Draw and explain Complementary Push-Pull Power Amplifier. 6
  - (b) Define the term feedback. What is the difference between negative feedback and positive feedback? Why we don't use positive feedback in an amplifier? 6

OR

- Que-4
- (a) Why voltage amplifier cannot be used as power amplifier? What are the performance parameters of power amplifier? 6
  - (b) Explain Class B push-pull amplifier with necessary diagram. 6

- Que-5
- (a) Write a short note on Silicon Control Rectifier. 6
  - (b) Draw and explain VI characteristics of Field Effect Transistor. 5

OR

- Que-5
- (a) Enlist applications of following: 6  
BJT, FET, Thyristor, Oscillator, Power amplifier, UJT
  - (b) Write a short note on Uni-junction transistor. 5

- Que-6
- (a) Design Colpitt Oscillator for frequency of 10kHz. 4
  - (b) Give classification of power amplifier. 4
  - (c) Give difference between Push-Pull Power Amplifier and Complementary Push-Pull Power Amplifier. 4

-----END OF PAPER-----