

GANPAT UNIVERSITY
B.Tech Sem. IVth Biomedical & Instrumentation Engineering
Regular Exam May / June-2013
2BM 403: Digital Logic Circuits

Time: 3 Hours

Total Marks-70

Instructions:-

1. All the questions are compulsory.
2. Answer of each section must be written in separate answer books.
3. Figure to the right indicate marks.
4. Assume data, if needed.
5. Conventional terms / notations are used.

Section – I

Que.1

[12]

- a) Define: Digital, Analog, Bit, Byte, Nibble.
Compare analog and digital.
- b) Convert:
 1. $(101001010.1101)_2 = (\quad)_{10}$
 2. $(415)_8 = (\quad)_{10}$
 3. $(734)_{10} = (\quad)_8$

OR

Que.1.

[12]

- a) What is Boolean Algebra? Name the methods to reduce Boolean expression.
Explain principle of Boolean Algebra with necessary diagrams.
- b) Reduce using K-map:
 1. $f = \sum m(0,2,6,10,11,12,13) + d(3,4,5,14,15)$
 2. $f = \prod M(2,7,8,9,10,12)$

Que.2.

[11]

- a) State and prove basic laws of Boolean Algebra.
- b) Find minterm: $Y(A,B) = A' + B'$
Find Maxterm: $Y(A,B) = A(B' + A)B$

OR

Que.2

[11]

- a) DeMorganize: $Y(A,B) = (A+B)' \cdot (A'+B)'$
- b) Reduce : $f = A+B[AC + (B+C')D]$

Que.3.

[12]

- a) Reduce using Tabular method: $f = \sum m(0,1,6,7,8,9,13,14,15)$
- b) Realize an explain AND logic gate using DIODE LOGIC and TRANSISTOR LOGIC.
- c) Difference between Combinational Logic Circuit and Sequential Logic Circuit.

Section – II

Que-4

- a) Design Half and Full Adder circuits with necessary logic diagrams.
- b) Design 2-bit comparator.

[12]

OR

Que-4

- a) Design a full adder using demultiplexer.
- b) What is Sequential Circuit? Name types of Sequential Circuits and difference between them.

[12]

Que-5

- a) Draw and explain clocked S-R flip-flop with truth table.
- b) Name types of counter. Explain ring counter with necessary diagrams. Write limitation of it.

[11]

OR

Que-5


- a) Draw and explain Master Slave J-K flip-flop.
- b) Define: Shift Register. Give types of Shift Register. Explain any one of it.

[11]

Que-6

- a) What is flip-flop? Explain characteristics of flip-flop.
- b) Explain flash type ADC.
- c)

[12]

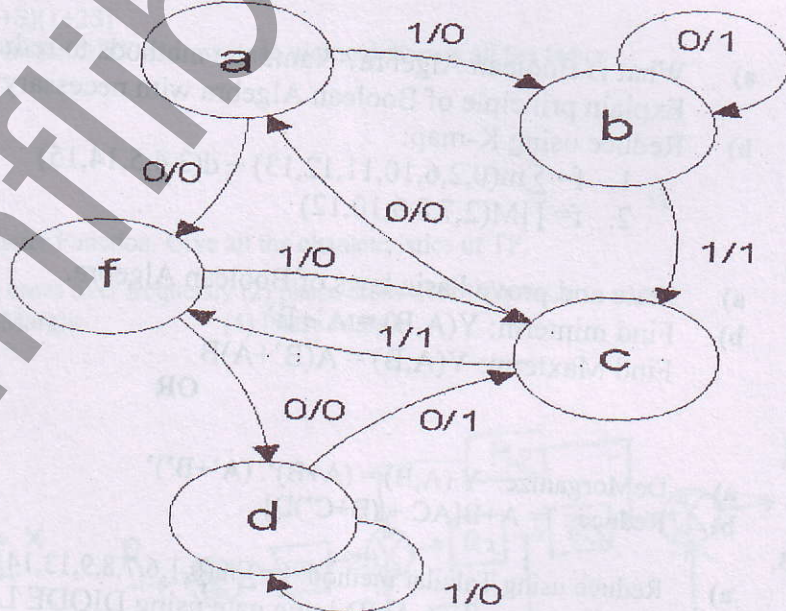

Design state table for the above state diagram. Use state reduction technique if possible.

‘END OF PAPER’