

GANPAT UNIVERSITY

B. Tech. Semester: IV (Biomedical & Instrumentation) Engineering

Regular Examination May – June 2014

2BM403 Digital Logic Circuits

Time: 3 Hours

Total Marks: 70

- Instruction: 1 Write each section in separate answer book.
 2 Answer should be brief and to the point.
 3 Figure to the right indicates marks.
 4 Assume suitable data, if necessary.

Section – I

Que. – 1

12

- a) Define basic logic gates and universal logic gates? Explain the universal gates with logic symbol and truth table.
 b) Implement an 8:1 Multiplexer using 4:1 Multiplexer.

OR

Que. – 1

12

- a) Convert the decimal number 357 in following code:
 i) Binary Code ii) Octal Code iii) BCD Code
 iv) Gray Code v) Excess -3 Code vi) Hexadecimal Code
 b) Draw the logic diagram of 2:4 Demultiplexer using NOR gate only.

Que. – 2

11

- a) Draw the Half & Full adder Circuit. Make a truth table for it. Also, draw the timing diagram for half adder circuit.
 b) Differentiate analog and digital system.
 c) Use a Karnaugh map to simply the following SOP expression:
 $B'C'D' + A'BC'D' + ABC'D' + A'B'CD + AB'CD + A'B'CD' + ABCD'$

OR

Que. – 2

11

- a) Differentiate BCD and Binary number system
 b) Using Boolean algebra techniques, simplify following expression:
 i) $(A' + B)(A + B + D)D'$
 ii) $AC' + BC'D + AB'C + ACD$
 c) Prove: i) $X'(X + Y) + Z' + ZY = Y + Z'$
 ii) $(B + A)(B + D)(A + C)(C + D) = BC + AD$

Que. – 3

12

- a) Answer in short:
 i) How many bits are required to represent three digit decimal numbers in BCD?
 ii) How many bits are needed to represent decimal values ranging from 0 to 14,556?


- iii) When is the output of AND gate is high? What is the IC number of 2 input AND gate?
- iv) Convert $(101101)_2$ to gray code.
- v) Enlist different non-weighted binary codes.
- vi) Which gate is known as inverter?
- vii) Find 2's complement of 10110010.
- viii) Determine the values of A, B, C and D that make the product term $A B' C' D$ equal to 1.
- b) Differentiate Combinational and Sequential circuit..
- c) Implement with logic gates: $A' B + B (A + C') + A B'$

Section – II

Que. – 4

12

 - a) Assume initially $Q = 0$, Determine Q and Q' waveform for NOR gate latch. Inputs are shown in below figure.



- b) Draw the logic symbol, logic diagram of J-K flip-flop and explain in detail.

OR

Que. – 4

12

- a) Draw and explain 2 bit asynchronous binary counter with timing diagram.
- b) What is the normal resting state of NAND gate as a latch? Explain in detail along with logic diagram and timing diagram.

Que. – 5

11

- a) What is the meaning of "SN 74 ALS 08 A" data written on IC? Draw RTL circuit for NOR gate operation and explain its working.
- b) Explain R-2R ladder type DAC.

OR

Que. – 5

11

- a) Draw and explain the circuit diagram of 1 bit memory cell. Also enlist the assumptions of it.
- b) What is the function of shift register? Draw and explain 4 bit serial in – serial out shift register.

Que. – 6

12

- a) What is the need of Preset and Clear in S-R flip-flop? Draw the symbol, logic diagram and explain.
- b) What is the meaning of "D" in D type flip-flop? What is its application? Draw the logic symbol, logic diagram and explain in detail.

END OF PAPER