

Date: 14/05/2016

Exam No: \_\_\_\_\_

**GANPAT UNIVERSITY**  
**B. TECH SEM- IV (BM&I) CBCS REGULAR EXAMINATION- APRIL-JUNE 2016**  
**2BM401: ANALOG INTEGRATED ELECTRONICS**

**TIME: 3 HRS**

**TOTAL MARKS: 60**

- Instructions:** (1) This Question paper has two sections. Attempt each section in separate answer book.  
(2) Figures on right indicate marks.  
(3) Conventional terms and notations are used.  
(4) Draw figures & circuits, write equations and assume data wherever necessary.

**SECTION: I**

**Q.1** **(10)**

- a) Define Integrated Circuits (IC). Differentiate between Analog and Digital IC's. Write its scale of integration. **5**
- b) Derive following equation for closed loop inverting amplifier given below: **5**

$$1) A_F = -\frac{R_F}{R_1} \quad 2) A_F = \frac{AK}{1 + AB}$$

Calculate output voltage for gain 10 and input voltage 2v.

**OR**

**Q.1** **(10)**

- a) Draw different configurations of Differential amplifier using transistor. What is single ended and double ended operation? **5**
- b) Explain integrator with neat circuit diagram and write equation for calculating frequency. **5**  
Draw the output waveform if input is sine and square wave.

**Q.2** **(10)**

- a) Describe how inverting configuration of OP-AMP can work as summing, scaling and averaging amplifier. Write output voltage equations. **5**
- b) Draw and explain circuit diagram of zero crossing detector. Draw input-output waveforms for non-inverting comparator of Op-Amp if input is 4v and Vref is +2V. **5**

**OR**

**Q.2** **(10)**

- a) What is Switching Mode Power Supply (SMPS)? Describe its working principle. **5**
- b) Write note on voltage controlled Oscillator. **5**

**Q.3** **(10)**

- a) Design first order High pass Butterworth filter at 1KHz cutoff frequency with pass band gain of 2. Plot its frequency response. Assume necessary data. **5**
- b) Draw differential amplifier with one Op-Amp. Derive equation of voltage gain. **5**



## SECTION: II

Q.4 (10)

- a) With the help of block diagram explain working of 555 timer as Monostable Multivibrator? 5
- b) Define: Filter. Give classification of filter. What are the advantages of active filter over passive filter? Write application of filter. 5

OR

Q.4 (10)

- a) Construct  $\pm 5$  V fixed power supply using voltage regulated IC. 5
- b) Explain working of sample and hold circuit using MOSFET. 5

Q.5 (10)

- a) Explain pin diagram of 555 timer and state its applications. 5
- b) Describe working of Instrumentation amplifier with circuit diagram and equations. Calculate the output voltage if inputs to amplifier is 6mv and 4mv respectively. Keep gain of amplifier 100. 5

OR

Q.5 (10)

- a) With the help of circuit diagram explain RC phase shift oscillator. Write equation to calculate frequency if R is  $10K\Omega$  and C is  $0.01\mu F$ . 5
- b) Define duty cycle. Write note on switching voltage regulator. 5

Q.6 (10)

- a) Write short note on: Square wave generator. 3
- c) Distinguish between signal generator, oscillator and function generator. 3
- b) Write note on V to I converter. 4

-----END OF PAPER-----