

## GANPAT UNIVERSITY

B. Tech. Semester: III (Computer Engineering)  
 Regular Examination November – December 2014  
 2CE302: Digital Electronics

Time: 3 Hours

Total Marks: [70]

## Instruction:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Answer both sections in separate answer sheets.

## Section – I

- Que.1 (A) Answer the followings. [5]
- (1)  $(101001011)_2 = (\quad)_{10}$
  - (2) Convert the decimal number 250.5 into base-3.
  - (3) Find the 9's complement of decimal number  $(1457)_{10}$
  - (4) Convert decimal number  $(8620)_{10}$  into excess-3 code.
  - (5) Perform Subtraction using 1's complement:  $(11001)_2 - (10101)_2$
- (B) State & prove the associative and distributive law. [4]
- (C) Express the Boolean function  $F = x + yz$  as a sum of minterm form [3]

OR

- Que.1 (A) Answer the followings. [5]
- (1)  $(630.4)_8 = (\quad)_{10}$
  - (2) Convert  $(1111)_2$  into gray code.
  - (3)  $(0.6875)_{10} = (\quad)_2$
  - (4)  $(FFF)_{16} = (\quad)_{10}$
  - (5)  $(673.12)_8 = (\quad)_2$
- (B) Express the boolean function  $F = y' + x'z'$  in a sum of minterm form and Product of maxterm form. [4]
- (C) Simplify the boolean function  $F = P + Q + R + R' + R$  using postulates. [3]

- Que.2 (A) Minimize the boolean function in product of sum form [3]  
 $F(A,B,C,D) = \sum (0,2,4,5,7,8,10,12,13,15)$  using Karnaugh map method
- (B) Minimize the boolean function in sum of product form using K-map [4]  
 $F(P,Q,R,S) = \sum (1,3,7,11,15)$  with don't care condition  
 $F(P,Q,R,S) = \sum (0,2,5)$
- (C) Explain Full adder combinational circuit. [4]

OR

- Que.2 (A) Minimize the boolean function in sum of product using K-map [3]  
 $F = A'B'C' + B'C'D' + A'BCD' + AB'C'$
- (B) Write short note on "octal to binary encoder". [4]
- (C) Explain Full subtractor combinational circuit. [4]

- Que.3 Answer the followings.
- (A) Simplify the boolean function using tabulation method [5]  
 $F(w,x,y,z) = \sum (0,1,2,8,10,11,14,15)$
- (B) Explain parity generator and parity checker circuit. [5]
- (C) Difference between combinational and sequential circuit [2]

Section – II

Que.4 (A) Answer the followings. [5]

- (1) What is the full form of MSI and LSI?
- (2) Define term carry propagation.
- (3) In D flip-flop when  $D=0$  and  $Q(t)=1$  then  $Q(t+1)=$  \_\_\_\_\_
- (4) How many selection lines are used in  $32 \times 1$  multiplexer?
- (5) In decoder input lines are 3 then how many output lines produce?

(B) Implement the following Boolean function with a Multiplexer. [4]

$$F(A,B,C,D) = \sum (0,1,3,4,8,9,15)$$

(C) Explain  $1 \times 8$  Demultiplexer in Details. [3]

OR

Que.4 (A) Answer the followings. [5]

- (1) Define term flip-flop.
- (2) When race conditions occur in R-S flip-flop?
- (3) What is difference between latch and register?
- (4) Define term trigger in the context of flip flop.
- (5) What is the full form of EPROM?

(B) Explain programmable Logic Array (PLA) in Details. [4]

(C) Discuss Master-Slave J-K Flip-Flop. [3]

Que.5 (A) Explain Serial adder in Register with block diagram. [6]

(B) Draw and Explain the block diagram of 4-bit full-adder with look-ahead carry. [5]

OR

Que.5 (A) Draw and explain 4-bit magnitude comparator circuit. [6]

(B) Write Short note on "Octal to Binary encoder". [5]

Que.6 (A) Write short note on  $8 \times 1$  multiplexer. [6]

(B) Discuss 4-bit Register with parallel loading using R-S Flip-Flop. [6]

END OF PAPER