

GANPAT UNIVERSITY
B. Tech Semester – III Information Technology
Regular Examination Nov - Dec 2012
2IT302: COMPUTER SYSTEM ORGANIZATION

Time: 3 Hours]

[Total Marks: 70

Instructions:

1. Attempt all questions.
2. Figures to the right indicate full marks
3. Each section should be written in a separate answer book

SECTION-I

1. (A) Answer the following [5]
- (1) Define term: Instruction.
 - (2) What is the difference between EEPROM and flash memory?
 - (3) Which function carried out by accumulator register?
 - (4) Define term: Microprocessor.
 - (5) Why microprocessor 8085 refer as 8-bit Microprocessor.
- (B) Explain 8085 microprocessor bus organization in brief. [4]
- (C) Explain flag register in brief [3]

OR

1. (A) Answer the following [5]
- (1) How many bits are used to represent memory address in 8085
 - (2) Which function is carried out by data bus?
 - (3) Which control signal is used to De-multiplex AD₀ – AD₇.
 - (4) When SIGN flag is set in 8085 microprocessor
 - (5) Which instruction is used to stop program execution?
- (B) Discuss 8085 registers in brief. [4]
- (C) Write an ALP to store 57H in register D and 1FH in register B. Perform addition on content of register D and B. Store result at memory location A001H. [3]
2. (A) Explain different type of memory in brief. [5]
- (B) Explain Following Instruction [6]
- (i) ADI (ii) LXI (iii) MVI

OR

2. (A) Draw and Discuss pin diagram of 8085 microprocessor. [5]
- (B) Explain Following Instruction. [6]
- (i) CMP (ii) XRI (iii) LDA
3. Answer the following (Any Three) [12]
- (1) Explain Arithmetic Micro-operation in brief.
 - (2) Discuss John Van Neumann model in detail
 - (3) Write a short note on "Five Generation of Computers"
 - (4) Write a short not on "Addressing modes"

[P.T.O]

SECTION-II

4. (A) Answer the following [5]
- (1) Convert $(9756.2)_{10}$ to binary number.
 - (2) Define term : Maxterm
 - (3) $(14D2)_{16} = (\quad)_{8}$
 - (4) How many flip- flops are used to design 6-bit register?
 - (5) Find gray code of $(101011)_2$.

(B) Prove $(A+B)' = A' \cdot B'$ and $(A \cdot B)' = A' + B'$ [4]

(C) Implement Boolean function $F = XY + XY'Z + X'Y' + X'$ using basic logic gates. [3]

OR

4. (A) Answer the following [5]
- (1) Convert $(1011110.11)_2$ to decimal number
 - (2) $(167)_8 = (\quad)_{16}$
 - (3) Define term : Minterm
 - (4) Perform $100001 - 10011$ using 1's complement method
 - (5) find 9's complement of $(234.25)_{10}$

(B) Minimize the following Boolean function [4]
 $F(W, X, Y, Z) = \Sigma(0, 1, 2, 3, 7, 8, 9, 11, 14, 15)$ using Karnaugh map method.

(C) Explain full adder in detail. [3]

5. (A) Explain combinational circuit which performs subtraction on two bits. [3]

(B) Write the difference between combinational and sequential circuit [4]

(C) Write a short note on "De- Multiplexer". [4]

OR

5. (A) Explain 3 X 8 decoder and also construct 4 X 16 decoder using 3 X 8 decoder [4]

(B) Discuss Tabulation method for to minimize Boolean function with an example [4]

(C) Explain 8 X 1 Multiplexer in detail [3]

6. Answer the following (Any Three) [12]

(1) Explain Master- Slave JK Flip- Flop in brief.

(2) Write a short not on "BCD Adder".

(3) Explain RS Flip – Flop in brief

(4) Discuss serial adder in detail.

----- END OF PAPER -----