

510/10/10
Date: 27/11/2014

Student Exam No. _____

GANPAT UNIVERSITY

B. Tech. Semester – III Information Technology
Regular Examination November- December, 2014
2IT302: Computer System Organization

IT

Time: 3 Hours]

[Total Marks: 70

Instructions:

1. Attempt all questions.
2. Figures to the right indicate full marks.
3. Each section should be written in a separate answer book.

SECTION-I

- Q-1 A. Convert the base of following numbers. Also show the process of conversion. [6]
1. $(123.45)_{10} = (\text{_____})_3$
 2. $(FA32B.A2)_{16} = (\text{_____})_8$
 3. $(10100100.1011)_2 = (\text{_____})_{10}$

- B. Express following functions in product of maxterm form. [6]
1. $F(A,B,C) = A(B+C)$
 2. $F(X,Y,Z) = XY + X'$

OR

- Q-1 A. Convert the following number base. Also show the process of conversion. [6]
1. $(10589.25)_{10} = (\text{_____})_2$
 2. $(123456.70)_8 = (\text{_____})_{16}$
 3. $(1100101.0101)_2 = (\text{_____})_8$

- B. Express following functions in sum of minterm form. [6]
1. $F(A,B,C) = (A+B)(A'+C)$
 2. $F(X,Y,Z) = XY + XZ'$

- Q-2 A. What is importance of parity bit in communication? Design odd parity generator circuit for 3 bit binary message. [5]

- B. What is binary parallel adder? Draw the circuit diagram of 4-bit binary parallel adder. [6]

OR

- Q-2 A. Design Octal to Binary encoder circuit. [3]

- B. Draw the circuit diagram for function $F(A,B,C,D) = A'BC + AD + A(B+CD)$. [3]

- C. Implement full adder circuit using suitable decoder and basic gates. [5]

- Q-3 A. Do as directed. [6]

1. Give reflected code of 10110.
2. Write 2's complement of 10000.
3. Write excess 3 code of 1010.
4. Write complement of $(A+B'C)$.
5. Write dual of $X+0 = X$.
6. Give 1's complement of 10010.

- B. Minimize the Boolean function $F(A,B,C,D) = \Sigma(0, 2, 4, 6, 8, 10, 12, 14) + d(1,5,13,9)$ using K-map method. [6]

SECTION-II

- Q-4 A. Design a counter that counts 00 to 11 using D flip-flop. [6]
B. Simplify function $F(W,X,Y,Z) = \sum(0,4,5,6,10,12,14,15)$ using tabular method. [6]

OR

- Q-4 A. Implement and explain master slave flip-flop in detail. [6]
B. Design a circuit for following function using multiplexer. [6]
 $F(X,Y,Z) = \sum(1,2,4,7)$

- Q-5 A. A memory location C202 contains 43 data. Write an ALP to convert this data to 34. [5]
Store the modified number to location D250.
B. Load the accumulator by 65 and get another number from memory location C300. [6]
Add these two numbers. If carry is generated then store 01 to register D otherwise store 02 to register D.

OR

- Q-5 A. A memory location D255 contains DA data. Mask the bits D0, D1, D2 and D5 of the [5]
given data and store result to memory location C261.
B. Subtract two number stored at memory locations C201 and C250. If result of [6]
subtraction is zero then store 01 to register H otherwise store 02 to register H.

- Q-6 A. Answer the followings. [8]
1. How many memory locations can be addressed using 10 bits?
2. How many bits require to access 2048 memory locations?
3. Write two 3-bytes instructions of 8085.
4. What is the size of data bus and address bus of 8085 microprocessor?
B. Identify addressing modes (Direct or Indirect or Immediate) for following 8085 [4]
instructions.

- | | |
|-------------|-------------|
| 1. SUB B | 3. LDAX B |
| 2. LDA 2300 | 4. MVI A,33 |

END OF PAPER