

GANPAT UNIVERSITY

**B. TECH. SEMESTER III ELECTRONICS & COMMUNICATION ENGINEERING
REGULAR EXAMINATION, NOV-DEC 2011**

2EC305 NETWORK ANALYSIS

Time: 3 HOURS.

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Answers to the two sections must be written in separate answer books.
3. Figures to the right indicate full marks. Assume suitable data, if necessary.

SECTION-I

- | | | | |
|---|-----|--|---|
| 1 | (A) | Derive the general solution for second order equation(Internal excitation) | 4 |
| | (B) | Determine the mesh Currents i_1, i_2 and i_3 in a network of fig.(1) | 6 |
| | (C) | In the Fig.(2) Obtain the voltage output across R_L | 2 |

OR

- | | | | |
|---|-----|---|---|
| 1 | (A) | In the network of fig. (3), a steady state is reached with the switch k open. At $t=0$, the switch k is closed. Find $i(t)$ (particular solution) | 6 |
| | (B) | Explain the classification of filter. | 4 |
| | (C) | Find the power dissipated in the 100Ω resistor and find the voltage rating of the dependent Source in fig.(4) | 2 |

- | | | | |
|---|-----|--|---|
| 2 | (A) | Explain Constant k-High pass filter with the attenuation band and Characteristic Impedance | 6 |
| | (B) | Find the loop Currents i_1, i_2 and i_3 in the network of fig. (5) | 5 |

OR

- | | | | |
|---|-----|---|---|
| 2 | (A) | Determine the voltage at each node for the circuit shown in Fig.(6) | 5 |
| | (B) | Explain and draw equivalent circuit for Resistor, inductor and capacitor In term of the initial & final Condition | 4 |
| | (C) | V-I relationship of R, L and C element | 2 |

- | | | | |
|---|-----|--|---|
| 3 | (A) | Explain Unilateral and Bilateral element with an example. | 4 |
| | (B) | Explain the tree branch voltage. Find for Given network in fig.(7) | 6 |
| | (C) | What is the Source transformation with an example? | 2 |

SECTION-II

- | | | | |
|---|-----|--|---|
| 4 | (A) | State and prove maximum power transform theorem. | 6 |
| | (B) | State norton's theorem. Find the current in 5Ω resistor using Norton theorem for fig. (1) | 6 |

OR

- | | | | |
|---|-----|--|---|
| 4 | (A) | State thevenin theorem. Find V_{th} and R_{th} for following network in fig. (2) | 6 |
| | (B) | Show validity of reciprocity theorem in fig. (3) and (4) | 6 |

- | | | | |
|---|-----|--|---|
| 5 | (A) | Determine $i_2(t)$ using Laplace transformation in the fig. (5), If switch 'K' is closed at time $t=0$. | 6 |
|---|-----|--|---|

- | | | | |
|--|-----|---|---|
| | (B) | Obtain $V(S)$ of the given waveform in fig. (6) | 5 |
|--|-----|---|---|

OR

- 5 (A) State relation between $u(t)$, $r(t)$ and $\delta(t)$, and prove it. 4
 (B) Obtain Y-parameters in terms of Z-parameters. 5
 (C) Define inverse H-parameters and give equation of it. 2
- 6 (A) For the resistive two port network of fig. (7). Determine the numerical values 6
 for G_{12} , α_{12} , Z_{12} , Y_{12} .
 (B) Prove the conditions for the network to be reciprocal and symmetry using Z- 4
 parameters.
 (C) Define poles and zeros of network function. 2

SECTION-I



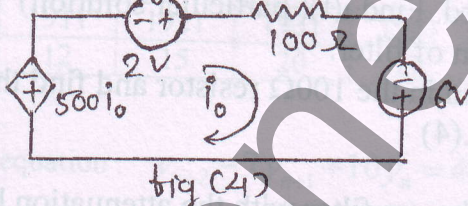
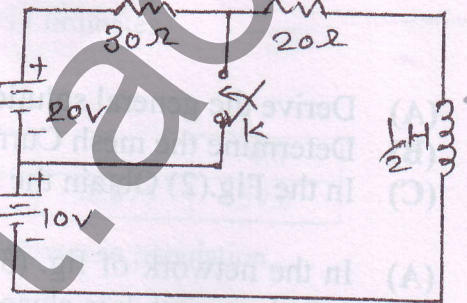
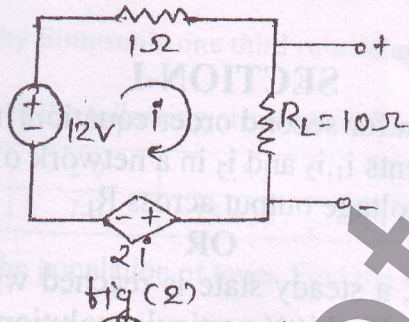
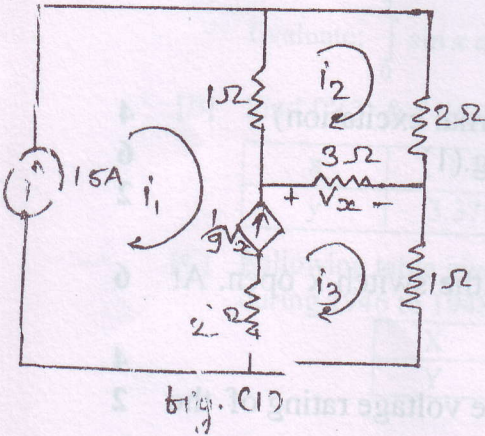
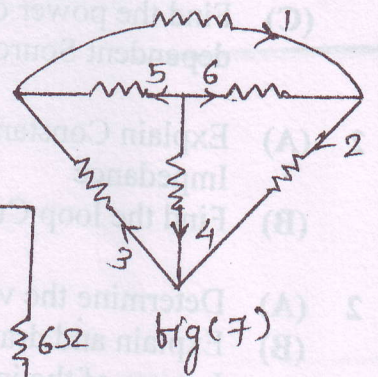


fig. (3)

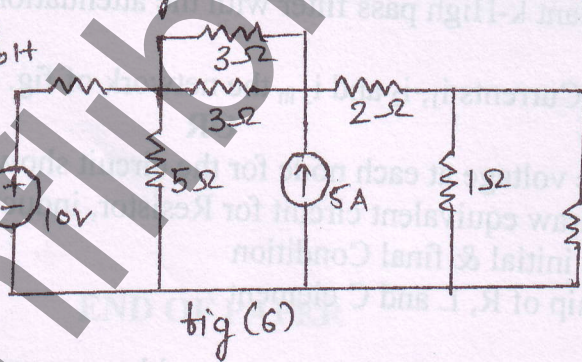

SECTION II

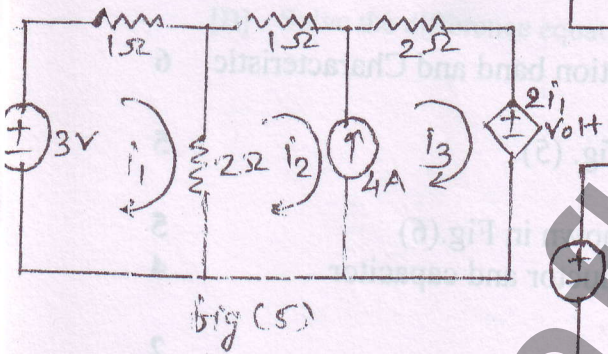