

GANPAT UNIVERSITY
B. TECH. SEMESTER III ELECTRONICS & COMMUNICATION ENGINEERING
CBCS NEW REGULAR EXAMINATION, NOV- DEC 2015
2EC303 NETWORK ANALYSIS

Time: 3 HOURS.

TOTAL Marks: 60

Instructions:

1. Attempt **all** questions.
2. Answers to the two sections must be written in **separate** answer books.
3. Figures to the right indicate full marks. Assume suitable data, if necessary.

SECTION-I

- Q.1 (A) State and prove maximum power transfer theorem for DC circuits. 5
- (B) Use Superposition theorem to find the value of 'V' across 20Ω resistor in the network of figure 1. 5

OR

- Q.1 (A) State and prove Norton theorem with necessary example. 5
- (B) State reciprocity theorem and by applying the reciprocity find the current through 1Ω Resistor in the shown figure 2 5

- Q.2 (A) Obtain Y parameter in terms of Z-Parameters 5
- (B) Describe about Attenuators. Design a Π type attenuator to give 20 dB attenuation and to have a characteristic impedance of 100Ω . 5

OR

- Q.2 (A) Describe about Attenuators. Design a T type attenuator to give 20 dB attenuation and to have a characteristic impedance of 100Ω . 5
- (B) What do you mean by Equalizer circuits? In detail explain about series equalizer circuit. 5
- Q.3 (A) List out various two port parameters for circuit analysis purpose. Discuss the concept of ABCD parameters for 2 stage two port cascaded circuit. 5
- (B) What is filter? Discuss about classification of filters in detail. 5

SECTION-II

- Q.4 (A) Find the currents through the all resistors shown in figure 3 using mesh analysis. 5
 (B) Explain the link Current and the tie-set schedule table & equation with an example. 5

OR

- Q.4 (A) Use nodal analysis to determine the current I in the network shown figure 4 5
 (B) Discuss about the source transformation and different network simplification techniques. 5

- Q.5 (A) Explain and obtain Laplace transform of unit step function and shifted unit step function 5
 (B) Obtain $f(s)$ of the given triangular waveform $f(t)$ in figure 5. 5

OR

- Q.5 (A) Find the Solution of a non-homogeneous Equation Using Integrating factor 5
 (B) In the network of the figure 6, the switch k is opened at $t=0$. Find the values of v , $\frac{dv}{dt}$ 5

$\frac{d^2v}{dt^2}$ at $t=0+$. if $I=10A, R=10\Omega, L=1H$.

- Q.6 (A) Discuss behavior of Resistor, inductor and capacitor in initial & final Condition with necessary circuit diagram. 5
 (B) Derive the general solution for second order equation using Internal excitation 5

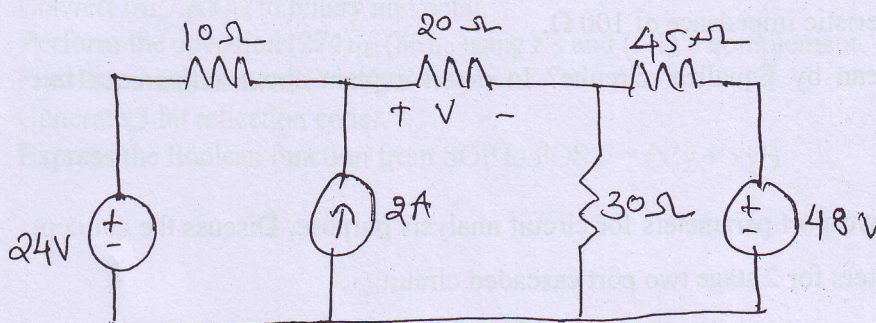


Figure-1

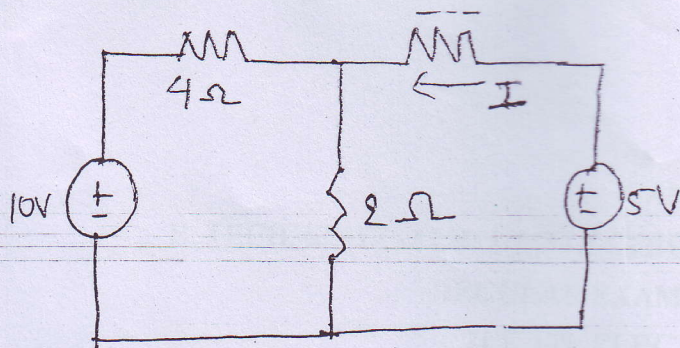


Figure-2

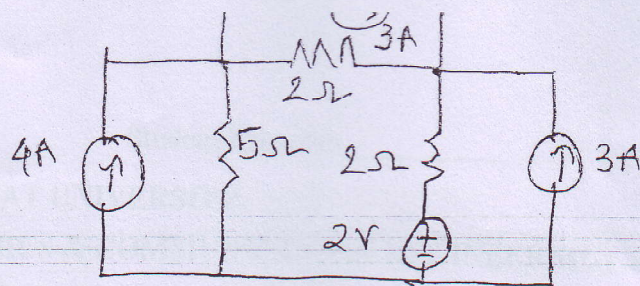


Figure-3

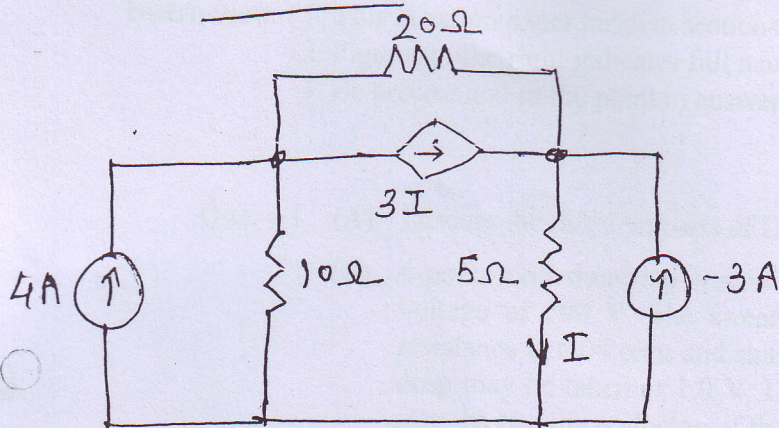


Figure-4

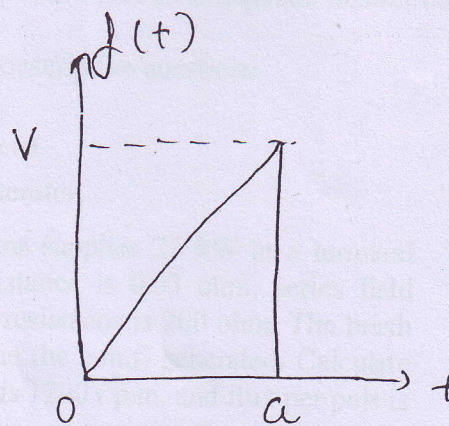


Figure-5

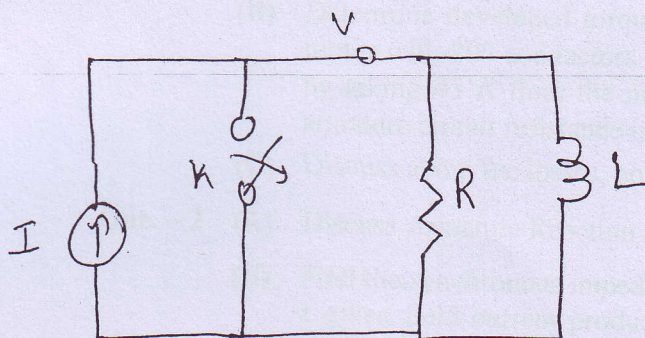


Figure-6

End of paper