

**GANPAT UNIVERSITY****B. Tech. Semester V Electronics & Communication Engineering****CBCS Regular Examination, December-2013****2EC503 Power Electronics & Applications****Time: 3 hours****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Answers to the two sections must be written in separate answer books.
3. Figures to the right indicate full marks.
4. Assume suitable data, if necessary.

**SECTION-I**

- Que.-1** (A) Explain reverse recovery characteristics of power diode and relate  $I_{RM}$  with  $Q_R$ . **6**
- (B) Draw and explain block diagram of power electronics control system in detail. **4**
- (C) Draw Symbol and characteristics of IGBT and GTO. **2**
- OR**
- Que.-1** (A) What is a Uni-junction transistor? Explain its configuration and characteristics. What is snow balling effect? **6**
- (B) List and explain various power electronic converter circuits in detail. **4**
- (C) Explain di/dt protection. **2**
- Que.-2** (A) Explain basic structure and two transistor model of thyristor. Derive equation for anode current. **6**
- (B) Explain static and dynamic equalizing network design for series operation of SCRs. **5**
- OR**
- Que.-2** (A) Explain resistance capacitance full wave triggering circuit in detail. **5**
- (B) Draw and explain switching characteristics of power BJT. **4**
- (C) Explain string efficiency. **2**
- Que.-3** (A) Explain working of TRIAC in all four modes. **5**
- (B) Write a short note on: operating principle of IGBT. **5**
- (C) Effects of freewheeling diode. **2**

## SECTION-II

- Que.-4 (A) Explain with neat circuit diagram and waveforms: Single phase half wave controlled rectifier circuit with R-L load with and without freewheeling diode. 7  
(B) Explain principle of step up chopper with related waveforms and equations. 5

OR

- Que.-4 (A) Explain with neat circuit diagram and waveforms: Single phase full wave controlled rectifier circuit (M-2 connection,  $\alpha=30^\circ$ ) with R-L load with and without freewheeling diode. 7  
(B) Explain class B chopper circuit with related waveforms. 5

- Que.-5 (A) Describe the working of a single phase half wave converter dc drives. 5  
(B) Write a short note on classification of inverters. 4  
(C) Draw possible configurations of single phase AC regulators. 2

OR

- Que.-5 (A) Explain with neat circuit diagram and waveforms: Single phase full bridge inverter circuit with R and R-L load. 6  
(B) What is UPS? Explain online and offline UPS with related block diagrams. 5

- Que.-6 (A) What is SMPS? List various types of SMPS and explain any one of them. 6  
(B) Explain principle of dual converter. 3  
(C) Calculate number of SCRs, each with rating of 500V, 75 A required in each branch of a series and parallel combination for a circuit with total voltage and current rating of 7.5kV and 1000A. Assume derating factor of 14%. 3

END OF PAPER