

## GANPAT UNIVERSITY

**B.Tech Semester VI, Electronics & Communication Engineering**  
**CBCS Regular Examination May-June 2014**  
**2EC606 Industrial Instrumentation**

Max. Time: 3 Hrs.]

[Max. Marks: 70

**Instructions:**

1. Attempt all questions.
2. Answers to the two sections must be written in separate answer books.
3. Figures to the right indicate full marks.
4. Assume suitable data, if necessary.

**SECTION-I**

- Que-1** (A) Compare the PLC and PC with regard to: 6
- |                                  |                          |
|----------------------------------|--------------------------|
| a. Physical hardware differences | c. Operating environment |
| b. Method of programming         | d. Execution of program  |
- (B) How Analog I/O Modules are different from discrete I/O modules? Explain in detail discrete I/O modules. 6

**OR**

- (A) Write a short explanation for each of the following analog I/O module specifications: 6
- |                              |                             |
|------------------------------|-----------------------------|
| a. Channels per module       | d. Nominal input voltage    |
| b. Nominal current per input | e. Resolution               |
| c. Electrical isolation      | f. Input threshold voltages |
- (B) Explain in detail different addressing format of Allen-Bradley PLC-5, SLC-500 and Logix5000 controllers. 6

- Que-2** (A) Write the Boolean expression and draw the gate logic diagram and typical PLC ladder logic diagram for a control system wherein a fan is to run only when all of the following conditions are met: 6
- Input A is OFF
  - Input B is ON or input C is ON, or both B and C are ON
  - Inputs D and E are both ON
  - One or more of inputs F, G, or H are ON
- (B) Explain operation of OTL and OTU instruction using suitable example. 5

**OR**

- (A) Draw block diagram of PLC processor module. Describe three typical modes of operation that can be selected by the key switch of a processor. 6
- (B) Compare the operation of the reflective type and through-beam photoelectric sensors. 5

- Que-3** (A) Draw and explain PLC program scan cycle. 4
- (B) Explain counter file and bit data file in brief. 4
- (C) Express each of the following equations as a ladder logic program: 4
- |                     |                                       |
|---------------------|---------------------------------------|
| a. $Y = (A + B) CD$ | b. $Y = [(\bar{A} + \bar{B}) C] + DE$ |
|---------------------|---------------------------------------|

**[Page Turn Over]**



## SECTION-II

- Que-1 (A) Draw the symbol and explain the operation of each of the following timed contacts of a mechanical timing relay with suitable example: 6  
a. On-delay timer-NOTC contact                      b. Off-delay timer-NOTO contact
- (B) Prepare typical I/O connection diagram and ladder logic program for the following counter specifications: 6
1. Counts the number of times a pushbutton is closed.
  2. Decrements the accumulated value of the counter each time a second pushbutton is closed.
  3. Turns on a light any time the accumulated value of the counter is less than 20.
  4. Turns on a second light when the accumulated value of the counter is equal to or greater than 20.
  5. Resets the counter to 0 when a selector switch is dosed.

OR

- (A) What determines the maximum speed of transitions that a PLC counter can count? Why? And Describe the basic programming process involved in the cascading of two counters using suitable example. 6
- (B) When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a program to implement this process. 6

- Que-2 (A) What types of instructions are not normally included inside the jumped section of a program? Why? Explain with suitable example. 6
- (B) Prepare PLC ladder logic program for following sequence (only use one timer). 5
- When the momentary start pushbutton is pressed solenoid A is energized immediately.
  - Solenoid B is energized 5sec later than solenoid A.
  - Solenoid C is energized 10sec later than solenoid A.
  - Solenoid D is energized 15sec later than solenoid A.

OR

- (A) A main conveyor has two conveyors, A and B, feeding it. Feeder conveyor A puts six-packs of canned soda on the main conveyor. Feeder conveyor B puts eight-packs of canned soda on the main conveyor. Both feeder conveyors have counters that count the number of packs leaving them. Construct a PLC program to give a total can count on the main conveyor. 5
- (B) State how the status of the output devices within the fenced zone will be affected when the MCR instruction makes a false-to-true transition and true-to-false transition. 5

- Que-3 (A) Compare continuous Processes and batch processes. 4
- (B) Explain the function of a sequencer input and sequencer compare instruction. What is the difference between SQI and SQC instructions? 4
- (C) Write a program that uses the FAL instruction to copy 20 words of data from the integer data file, starting with N7:40, into the integer data file, starting with N7:80. 4

=====END OF PAPER=====