

GANPAT UNIVERSITY
B.TECH SEM.3rd ELECTRICAL ENGINEERING
REGULAR EXAMINATION NOV-DEC 2012
2EE302: CIRCUIT ANALYSIS

TIME:-3 HOURS
INSTRUCTION:-

TOTAL MARKS-70

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Section-I

- Q-1** (a) Find the Laplace transform of the staircase type voltage waveform shown in figure 1. [06]
- (b) Determine the voltages of node 1 and node 2 in the network shown in figure 2 using input and output admittances. [06]

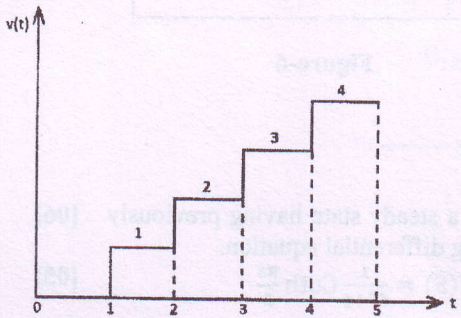


Figure-1

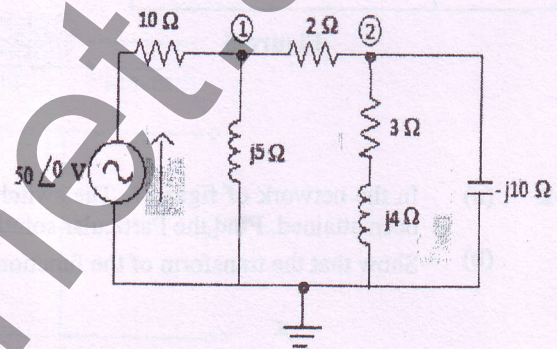


Figure-2

OR

- Q-1** (a) In the network shown in figure 3, a steady state is reached with switch k open. At $t=0$, the switch is closed. For the element values given, determine the value of $V_a(0^-)$ and $V_a(0^+)$. [06]
- (b) Determine the current through $j10\ \Omega$ impedance in a network of figure 4 using mesh current analysis. [06]

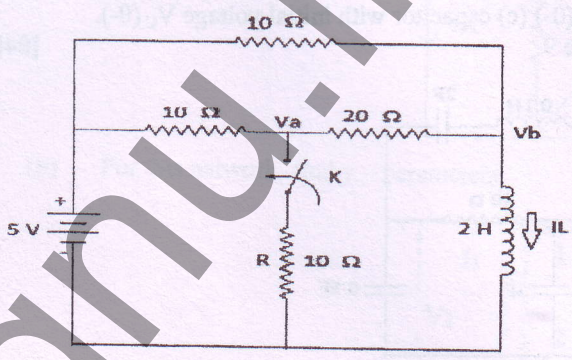


Figure-3

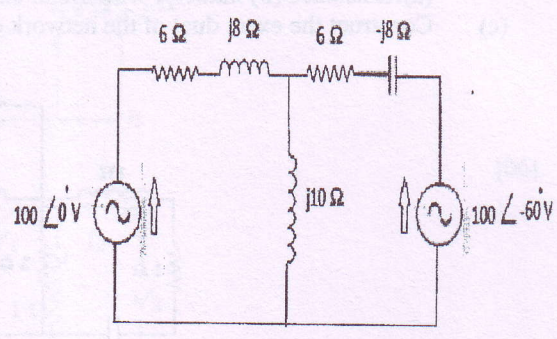


Figure-4

Q-2 (a) In the given circuit of figure 5, the switch K is moved from position a to b at time $t = 0$, the steady state having previously established. Find the particular solution for the current using Laplace transform method. [06]

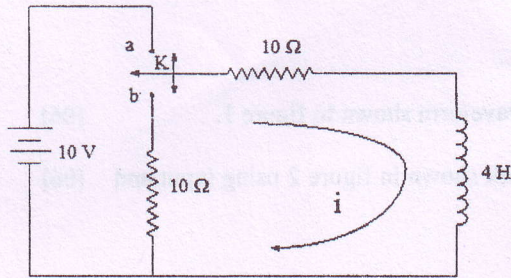


Figure-5

(b) In the network of figure 6, the switch k is moved from position a to position b at $t=0$ (a steady state existing in position a before $t=0$). Solve for the current $i(t)$ using the Laplace transformation method. [05]

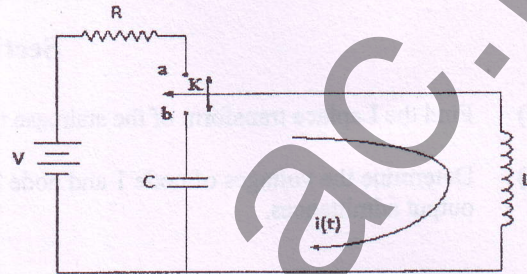


Figure-6

OR

Q-2 (a) In the network of figure 7, The switch K is closed at $t = 0$, a steady state having previously been attained. Find the Particular solution for the current using differential equation. [06]

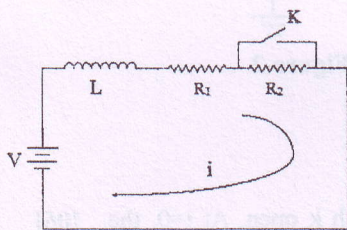


Figure-7

(b) Show that the transform of the function shown in figure 8 is $V(S) = \frac{1}{s^2+1} \text{Coth} \frac{\pi s}{2}$ [05]

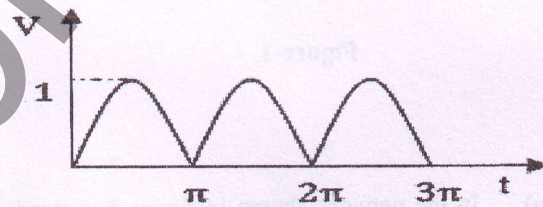


Figure-8

Q-3 (a) Explain the initial value theorem and final value theorem. [04]

(b) Draw and Explain the transform networks of the following elements [04]

(a) Resistance (b) inductor with initial current $I_L(0^-)$ (c) capacitor with initial voltage $V_C(0^-)$.

(c) Construct the exact dual of the network of figure 9. [04]


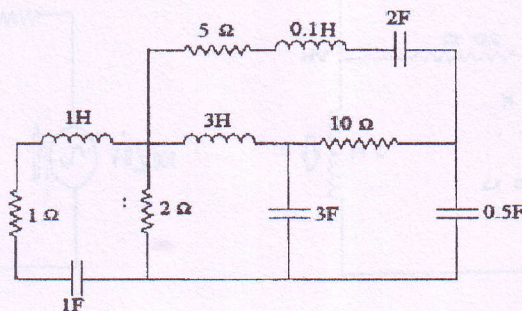


Figure-9


Section-II

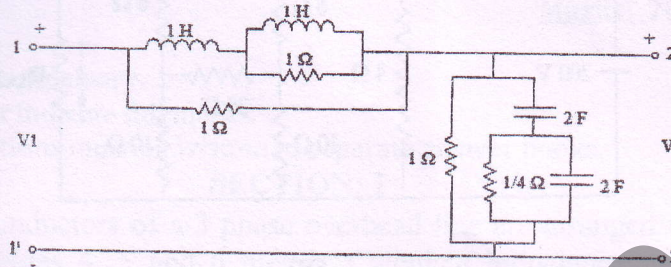- Q-4 (a) For the network of figure, show that with port 2 open, the input impedance at the port 1 is 1Ω . [06]
Also find the voltage ratio transfer function $G_{12}(s)$ for the two port network.



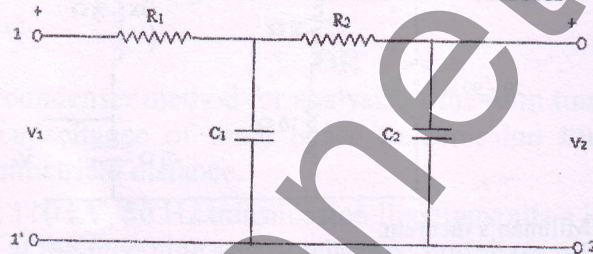
- (b) For R-C two port network shown in figure, show that

$$G_{12}(s) = \frac{1/R_1 R_2 C_1 C_2}{s^2 + \frac{(R_1 C_1 + R_1 C_2 + R_2 C_2)s + 1}{R_1 R_2 C_1 C_2}}$$




OR

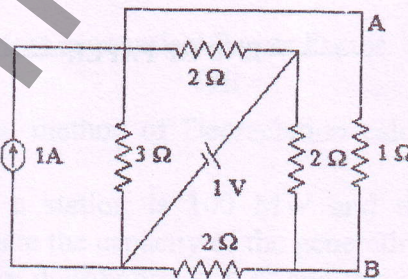
- Q-4 (a) Determine the current in 1Ω resistor of the network shown in below Figure, using Norton's theorem. [06]



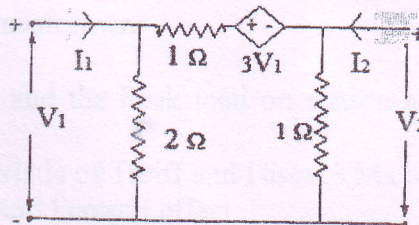- (b) For this network, find y-parameters.




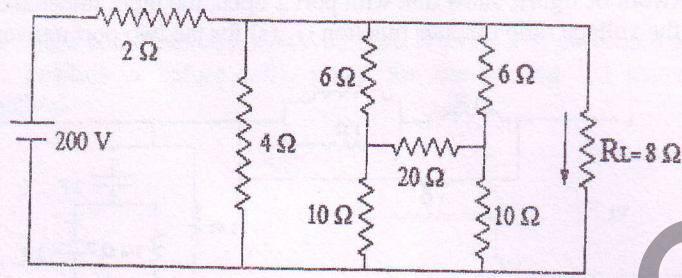- Q-5 (a) Explain Symmetry and Reciprocity condition in terms of y-parameters. [05]
 (b) Find the current through a load of 8Ω in the circuit of below figure, with the help of Norton's theorem. [06]



OR

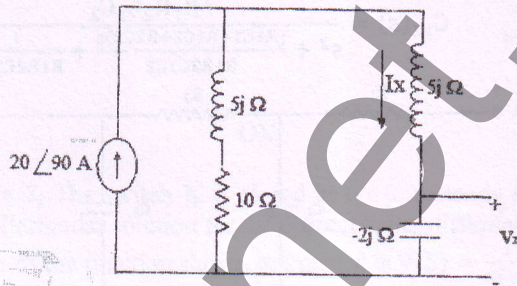- Q-5 (a) In the network of below figure, determine the voltage V_x . Then apply the reciprocity theorem and compare the two voltages. [06]



- (b) State and explain Millman's theorem. [05]
- Q-6 (a) Why do negative sign appear in the performance equations of a two port network in terms of ABCD-parameters? [04]
 (b) Write the performance equation and draw an equivalent circuit of a two port network in terms of g- parameters. [04]
 (c) Explain: (1) High-pass filter (2) Band-pass filter [04]

-----END OF PAPER-----