

**GANPAT UNIVERSITY**  
**B.TECH SEM.3<sup>rd</sup> ELECTRICAL ENGINEERING**  
**REGULAR EXAMINATION NOV-DEC 2012**  
**2EE302: CIRCUIT ANALYSIS**

TIME:-3 HOURS

TOTAL MARKS-70

INSTRUCTION:-

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

**Section-I**

- Q - 1 (A) In the given circuit of fig 1, the switch K is moved from position a to b at time  $t = 0$ , the steady state having previously established. Find the particular solution for the current using Laplace Transform method. [6]
- (B) In a network shown in fig 2, a steady state is reached with switch k open. At  $t=0$ , the switch is closed. Determine the values of  $V_a(0^-)$ ,  $V_a(0^+)$ ,  $V_b(0^-)$  and  $V_b(0^+)$ . [6]

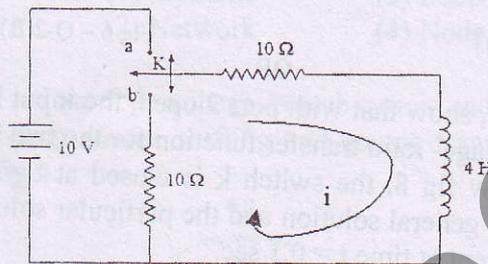


Fig 1-Q-1 (A)

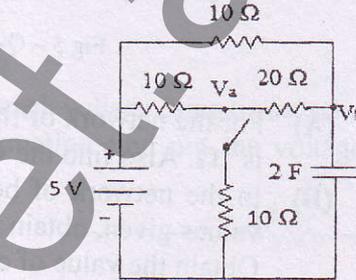


Fig 2-Q-1(B)

OR

- Q - 1 (A) In the network of fig3, The switch K is changed from position 1 to 2 at  $t = 0$ . Find values of  $i$ ,  $di/dt$  and  $d^2i/dt^2$  at  $t = 0$ . [6]

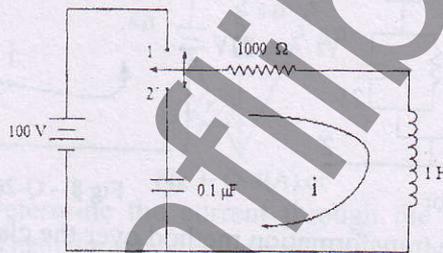


Fig 3-Q-1(A) or

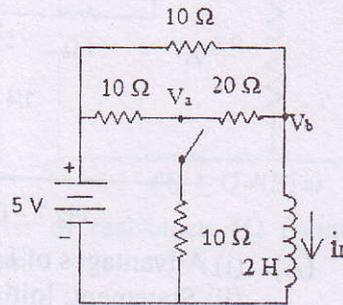


Fig 4-Q-1(B) or

- (B) In the network shown in fig 4, a steady state is reached with switch k open. At  $t=0$ , the switch is closed. Obtain particular solution for  $V_a$  at node a for  $t > 0$ . using differential equation method. [6]

Q-2 (A) For the waveform shown in below fig 5, write its equation and determine its Laplace transform. [5]

(B) For R-C two-port network shown in below fig 6, show that [6]

$$G_{12} = \frac{1/(R_1 R_2 C_1 C_2)}{S^2 + \frac{(R_1 C_1 + R_1 C_2 + R_2 C_2)S}{R_1 C_1 R_2 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}$$

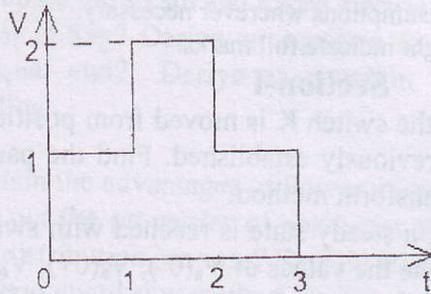


Fig 5 - Q-2(A)

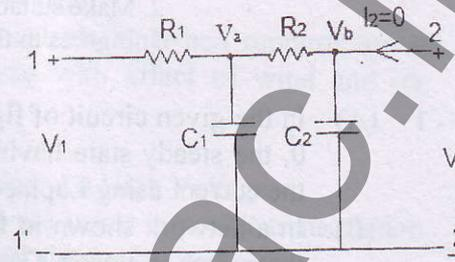


Fig 6 - Q-2(B)

OR

Q-2 (A) For the network of fig 7, show that with port 2 open, the input impedance at port 1 is  $1\Omega$ . Also find the voltage-ratio transfer function for the two port network. [6]

(B) In the network of below fig 8, the switch k is closed at  $t = 0$ . For the element values given, obtain the general solution and the particular solution for current  $i(t)$ . Obtain the value of current at time  $t = 0.1$  sec. [5]

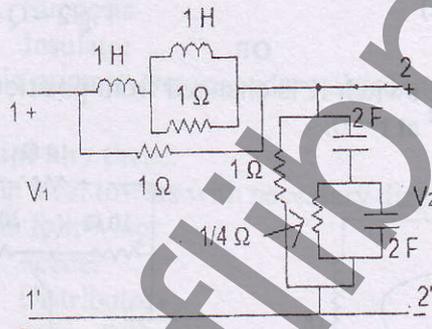


Fig 7 - Q-2(A) or

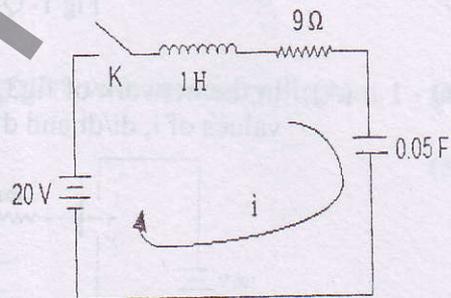


Fig 8 - Q-2(B) or

Q-3 (A) (i) Advantages of Laplace transformation method over the classical methods. [4]

(ii) Statement: Initial and final value theorem.

(B) Explain: (i) High pass filter (ii) Band stop filter [4]

(C) Draw and Explain the transform networks of the following elements (i) Resistance [4]

(ii) inductor with initial current  $I_L(0-)$  (iii) capacitor with initial voltage  $V_C(0-)$

### Section-II

- Q-4 (A) Write the mesh equation and find the mesh current  $I_X$  for fig 1. [4]  
 (B) Find the current through various resistance in the network as shown in fig 2 using nodal analysis. [4]

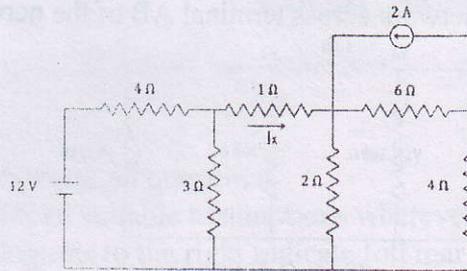


Fig 1- Q-4(A)

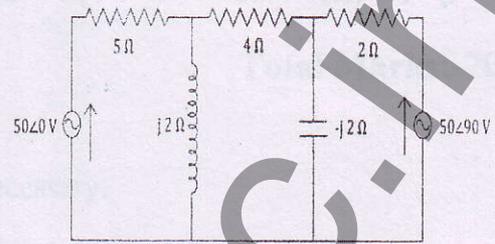


Fig 2- Q-4(B)

- (C) Define Following. [4]  
 (1) Element (3) Loop  
 (2) Network (4) Node

OR

- Q - 4 (A) Find the node voltage, branch current and branch voltage using tie set schedule fig 3. [8]  
 (B) Using source shifting and source transformation find out the voltage  $V_X$  in the fig.4 [4]

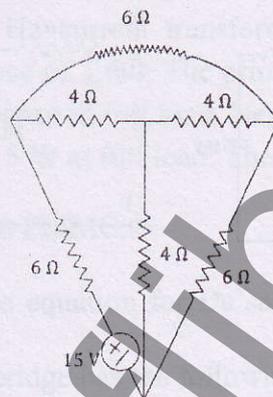


Fig 3- Q-4(A) or

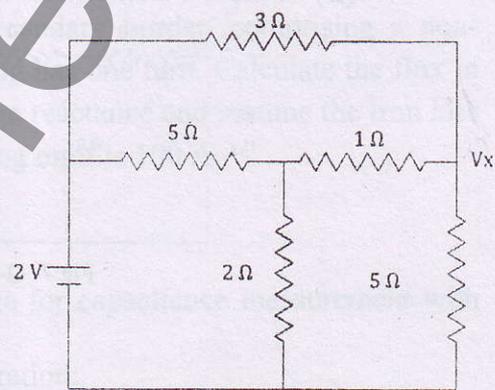


Fig 4- Q-4(B) or

- Q - 5 (A) Determine the current through the ammeter of resistance  $4\Omega$  connected in the Wheatstone bridge using Thevenin's theorem. [6]

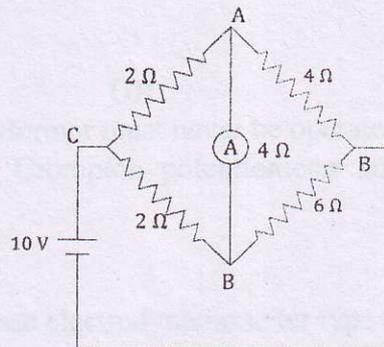


Fig 5- Q-5(A)

- (B) State the Maximum Power transfer theorem and derive the condition when load consists of a variable resistance. [5]

OR

- Q - 5 (A) Find Norton's equivalent network across terminal AB of the network shown in fig [6]

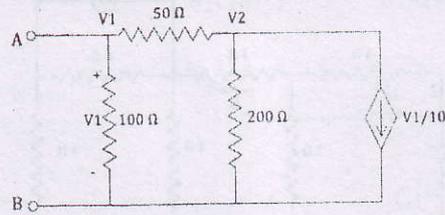


Fig 6- Q-5(A) or

- Q - 6 (B) Explain Reciprocity theorem with suitable example. [5]  
 Answer the following question. Any Three [12]
- (A) Discuss the Z parameter for two port network and derive the condition for reciprocity and symmetry network.
- (B) Find H Parameter for a given network as shown in fig 7 and find whether the network is reciprocity or not.
- (C) Give the relation between Z parameter and Y parameter.
- (D) Find Y Parameter for fig 8 and find whether the network is reciprocity or not.

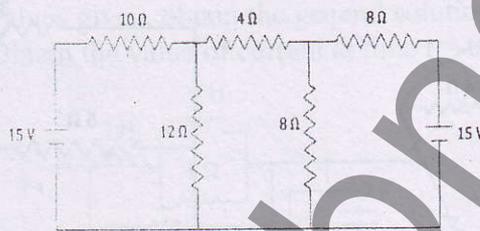


Fig 7- Q-6(B)

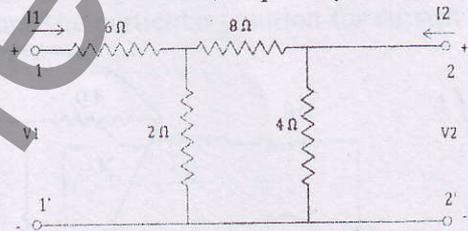


Fig 8- Q-6(D)

END OF PAPER