Student Exam No:-

GANPAT UNIVERSITY B.TECH SEM-V (ELECTRICAL) REGULAR EXAMINATION NOV-DEC-2015 2EE503:- POWER ELECTRONICS DEVICES & CIRCUITS

Time: 3 Hours

1

Total Marks:-70

[06]

[12]

Instructions: - 1. Attempt all questions.

- 2. Make suitable assumptions wherever necessary.
- 3. Answer to two sections must be written in separate answer books.
- 4. Figures to the right indicate full marks.

SECTION-I

- Que.-1 (A) Define: AC voltage regulator. Explain the working of an AC voltage regulator [06] with Integral Cycle Control.
 - (B) What is mid-point cycloconverter? Explain its working with input and output [96] waveforms.

OR

- Que.-1 (A) Draw the various possible configuration for single phase AC voltage regulator. [06]
 - (B) The resistance of a heating element of a 230 V, 5 kW resistance furnace is 12 [06]
 Ω. Find:(1) The duty ratio, for 50% input power using Integral Cycle Control
 (2)The duty ratio, for 50% of the rated voltage using Integral Cycle Control
 - (3)Power factor for condition (2).
- Que.-2 (A) What are the methods for controlling the output voltage of an inverter? Discuss [05] series inverter control.
 - (B) Draw the gate pulses, line to line voltage and phase voltage waveforms [06] regarding to 120^o conduction mode.

OR

Que.-2 (A) Explain SPWM technique of inverter voltage control.

(B) A three-phase bridge inverter is fed from a 450 V DC source. The inverter is [05] operated in 180⁰ conduction mode and is supplying a purely resistive star connected load. Determine: a) RMS value of the output line & phase voltages.
b) RMS value of load current and power delivered to the load if the load resistance is 20 Ω/phase.

Que.-3

- Attempt any three:
- (A) Draw and explain any one type of SMPS with neat sketch.
- (B) What are the types of UPS? Draw line diagram of any two methods of it.
- (C) Compare: Thyristor and Transistor.
- (D) Calculate the number of SCRs, Each with rating of 500 V, 75A required in each branch of a series and parallel combination for a circuit with the total voltage and current rating of 7.5 KV and 1000A. Assume derating factor of 14%

SECTION-II

- Que.-4(A)With proper graphical representation, explain characteristic of Thyristor.[06](B)What is forced commutation? Explain operational modes of class C and class D[06]
 - (B) What is forced commutation? Explain operational modes of class C and class D for commutation circuit in detail.

OR

- Que.-4 (A) Why series and parallel connection of SCR is required? Explain equalization [06] techniques for series and parallel connection. [06]
 - (B) Describe following protection scheme with proper circuit diagram:
 - 1. di/dt protection
 - 2. dv/dt protection
 - 3. Gate protection
- Que.-5 (A) Derive average output voltage equation for single phase half wave fully [0 controlled rectifier for RL load and draw waveform for output voltage Vo, output current Io and voltage across Thyristor.
 - (B) With the help of circuit diagram and waveforms explain three phase half wave [05] fully controlled rectifier.

OR

- Que.-5 (A) What is effect of source impedance on the performance of the single phase full [06] wave fully controlled rectifier? Explain with circuit diagram and waveform also derive average output current equation for this case.
 - (B) A delayed full wave rectified current for resistive load has an average value [05] equal to half of its maximum value. Find the delay angle α. Also draw circuit diagram and waveform.
- Que.-6

Attempt any three:

- (A) Explain basic operation of step up chopper and derive equation for output voltage Eo.
- (B) Classify chopper on the basis of direction of Eo and Io also describe its operational modes of class C chopper.
- (C) Draw circuit diagram of multiphase chopper and explain its operation with the help of waveforms.
- (D) 1. A step up chopper is used to deliver load voltage of 500 v from a 220 v dc source. If the blocking period of the Thyristor is 80 μs, compute the required pulse width.

2. A DC copper operates on 230 V dc and frequency of 400 Hz, feeds an RL load. Determine the ON time of the chopper for output of 150 V.

END OF PAPER

[12]