

## GANPAT UNIVERSITY

## B. Tech. Semester: VII (Electrical Engineering)

Regular Examination Nov-Dec 2015

## Subject: Advanced Power Electronics (2EE 721)

Time: 3 Hours

Total Marks: 70

- Instruction: 1 Draw neat sketch wherever required.  
 2 Assume suitable data if required.  
 3 Figures to the right indicate full marks.

## Section - I

- Que.-1 (a) Why gate drive circuit is required? Discuss use of pulse transformer for the same. 6  
 (b) Distinguish linear voltage regulators with switched mode voltage regulators. Explain working principle of boost converter with neat sketch and waveforms. 6

## OR

- Que.-1 (a) What are Opto-isolators? Explain gate drive circuit for IGBT. 6  
 (b) Explain working principle of buck-boost converter with neat sketch and waveforms. 6

- Que.-2 (a) Distinguish multi pulse converter and multi level converter. Explain transformer connections of 12 pulse converters. 5  
 (b) Explain working principle of CUK converter with neat sketch and waveforms. 6

## OR

- Que.-2 (a) With neat circuit diagram explain working principle of 18 pulse converters. 5  
 (b) Explain working principle of SEPIC converter with neat sketch and waveforms. 6

- Que.-3 Attempt any two: 12  
 (a) Explain zero crossing detection principle.  
 (b) Mention different schemes for gate firing. Explain any one.  
 (c) Explain applications of DC-DC converters.

Section – II

- Que.– 4 (a) Explain sine PWM technique. Draw harmonic profile of the same for 12  
the ratio  $f_c/f_m = 15$ .
- (b) What is carrier based PWM technique. Explain it in details.

OR

- Que.– 4 (a) What is PWM? Why is it required? Discuss hysteresis band PWM 12  
controller.
- (b) Discuss concept of SVPWM technique. How it is better than sine PWM  
technique?

- Que.– 5 (a) Distinguish CSI and VSI. Discuss their applications. 5
- (b) Explain 3 level flying capacitor inverter. 6

OR

- Que.– 5 (a) Distinguish line commutated inverters and load commutated inverters. 5  
Discuss their applications.
- (b) Explain 3 level diode clamped inverter. 6

- Que.– 6 Attempt any two: 12
- (a) Explain reduction of harmonics in inverter output voltage.
- (b) Explain 3 level cascaded H bridge inverters.
- (c) Discuss 3-phase series inverters.

END OF PAPER