

GANPAT UNIVERSITY
B.TECH SEM. IV - MECHATRONICS ENGINEERING
CBCS REGULAR EXAMINATION MAY/JUNE - 2013
2MC403/MC403 DIGITAL CIRCUITS & DEVICES

Time: 3 Hours

Total Marks: 70

Instructions:


- 1). All questions are **compulsory**.
- 2). Figures to the **right** indicate full marks.
- 3). Answers to the two sections must be written in **separate** answer books.
- 4). Assume all necessary data.

Section - I**Que:-1 Attempt All.****[12]**

- (A) Explain the master slave RS flip flop.
- (B) Explain direct inputs with example.
- (C) Explain successive approximation A/D converters.

OR**Que:-1 Attempt All.****[12]**

- (A) Explain serial Transfer from register A to register B.
- (B) Construct modulo 6 counter in two different ways.
- (C) Explain DAC.

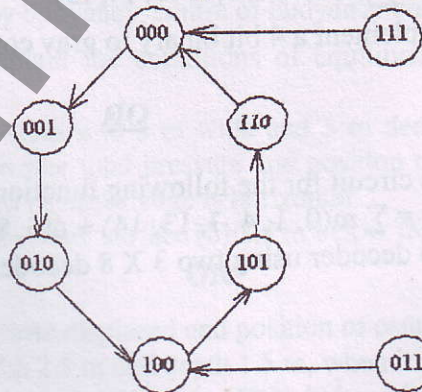Que:-2 (A) Design a counter for following state diagram. Use JK flip flops.**[07]****(B) Draw the logic diagram for 4-bit register with parallel load.****[04]****OR**

- Que:-2 (A) Design a BCD synchronous counter using T flip flop.**
- (B) Draw the logic diagram for 4 bit universal register.**

[07]**[04]**

Que:-3 Attempt All.

[12]

- (A) Which flip flop has an ability to toggle or change the state? Explain it.
- (B) Write down the excitation table for RS, JK, D and T flip flops.
- (C) Explain the RTL gate.

Section - II

Que:-4 Attempt All.

[12]

- (A) Simplify following by K-Map:

$$F(W, X, Y, Z) = \sum(1, 3, 7, 11, 15)$$

$$D(W, X, Y, Z) = \sum(0, 2, 5)$$

- (B) Explain full subtractor.
- (C) Prove that $(B + BC)(B + B'C)(B + D) = B$.

OR

Que:-4 Attempt All.

[12]

- (A) Solve using K-map.

$$F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$$

- (B) Implement the following function with a multiplexer.

$$F = A \oplus B \oplus C.$$

- (C) Show that $AB + (A + B)' = A \odot B$ by truth table.

Que:-5 (A) Solve by tabulation method.

[06]

$$F(A, B, C, D) = \sum(0, 1, 6, 7, 8, 9, 13, 14, 15).$$

- (B) Design and implement a 4 bit binary to gray converter.

[05]

OR

Que:-5 (A) Design a logic circuit for the following function using tabular method.

[07]

$$F(A, B, C, D) = \sum m(0, 1, 4, 7, 13, 14) + d(5, 8, 15)$$

- (B) Design 4 X 16 decoder using two 3 X 8 decoder.

[04]

Que:-6 Attempt All.

[12]

- (A) Multiply 1100_2 by 1001_2 using computer method.

- (B) Compare digital system V/S analog system.

- (C) Explain the equivalence logic gate.

- (D) Draw the logic diagram for AND, OR and NOT gate using NOR gate.

END OF PAPER