

GANPAT UNIVERSITY

B. Tech. Semester: IV Mechatronics Engineering

Regular Examination May 2014

2MC403 DIGITAL CIRCUITS & DEVICES

Time: 3 Hours

Total Marks: 70

Instruction:

- 1). All questions are compulsory.
- 2). Figures to the right indicate full marks.
- 3). Answers to the two sections must be written in separate answer books.
- 4). Assume all necessary data.


Section - I

- Que. - 1 Attempt all. 12
- A Design an 8 to 1 line multiplexer. 4
- B Solve following: 4
1. $x + x = x$
 2. $x + 1 = 1$
 3. $(x + y)' = x' \cdot y'$
 4. $x + x \cdot y = x$
- C Design a BCD to decimal decoder. 4
- OR
- Que. - 1 Attempt all. 12
- A Implement the following function by MUX. 4
- $$F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$$
- B Design and explain a 4 bit BCD adder. 4
- C Solve the following by tabulation method & compare answer with K-map. 4
- $$F(A, B, C, D) = \sum (0, 1, 2, 8, 10, 11, 14, 15)$$
- Que. - 2 Attempt all. 11
- A Design and explain Excess 3 to BCD code converter using MSI. 4
- B Discuss the various types of logic gates in detail. 4
- C Explain the concept of priority encoder. 3
- OR
- Que. - 2 Attempt all. 11
- A Discuss the concept of carry propagation and solution for the same. 4
- B Explain 4-bit binary to grey code converter. 4
- C Design a half subtractor circuit. 3
- Que. - 3 Attempt all. 12
- A Design & explain magnitude comparator. 4
- B Design & implement a full adder with its implementations. 4
- C Simplify the following Boolean function using K-map. 4
- $$F(A, B, C, D, E) = \sum (0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$$

Que. - 4 Attempt all.

12
6

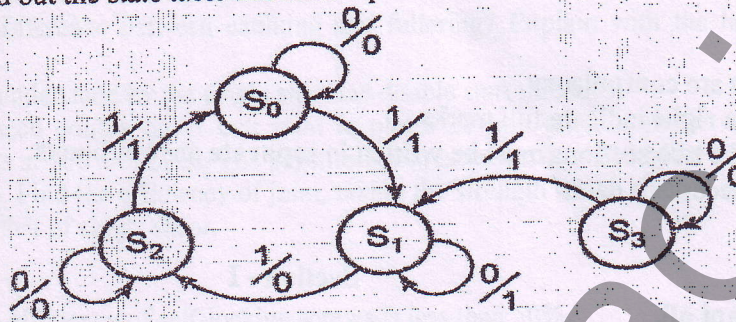- A With the use of the excitation table carry out the following conversion:
1. SR to JK
 2. SR to D
 3. T to JK
 4. D to SR
- B Find out the state table and state equations for the figure.




OR

Que. - 4 Attempt all.

12
6
6

 
- A Design the binary counter having the following repeated sequence 0,1,3,2,6,4,5,7 continuously. Use RS flip flop.
- B Find out the state table and state equations for the figure.



Que. - 5 Attempt all.

11
6

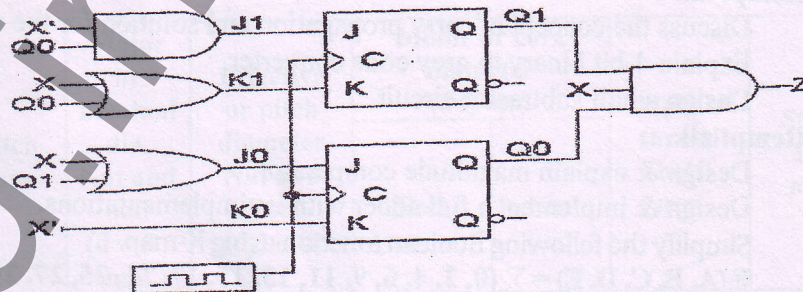- A Do the analysis of the circuit given in figure.



- B A sequential circuit with two D flip-flops, A and B; two inputs, x and y; and one output, z, is specified by the following next-state and output equations:

5

$$A(t+1) = x'y + xA$$

$$B(t+1) = x'B + xA$$

$$z = \dot{B}$$


- (a) Draw the logic diagram of the circuit.
- (b) List the state table for the sequential circuit.
- (c) Draw the corresponding state diagram.

Que. - 5 Attempt all.

11

A Do the analysis of the circuit given in figure.

6

 

B A sequential circuit has two JK flip-flops A and B and one input x. The circuit is described by the following flip-flop input equations:

5

$$\begin{aligned} J_A &= x & K_A &= B' \\ J_B &= x & K_B &= A \end{aligned}$$

- (a) Derive the state equations $A(t+1)$ and $B(t+1)$ by substituting the input equations for the J and K variables.
- (b) Draw the state diagram of the circuit.

Que. - 6 Attempt all.

12

- A
1. Convert $(325)_8$ to decimal.
 2. Convert $(78)_{10}$ to binary number.
 3. Perform subtraction using 1's complement.
 $(1010100)_2 - (1000011)_2$

6

B PN flip flop has four operations, no change, clear to 0, set 1 and compliment, when inputs P and N are 00,01,10 and 11 respectively.

2

1. Draw excitation table and truth table
2. Derive the characteristic equations.

C Reduce the number of states in the following state table and tabulate the reduced state table

4

Present state	Next state $x=0$	Next state $x=1$	Output $x=0$	Output $x=1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

END OF PAPER