

**GANPAT UNIVERSITY**  
**B.TECH SEM. IV BIOMEDICAL & INSTRUMENTATION ENGINEERING**  
**CBCS REGULAR EXAMINATION MAY/JUNE - 2015**  
**2BM401: ANALOG INTEGRATED ELECTRONICS**

Time: 3 hour

Marks: 70

**INSTRUCTION:**

1. Write each section in separate answer books.
2. All questions are compulsory.
3. Draw figures & circuits, write equations and assume data wherever necessary.
4. Conventional terms / notations are used.
5. Figure to the right indicate marks.

**Section – I**

- Q.1** [12]
- a) How triangular wave can be generated using comparator with necessary diagrams. Derive equation to calculate frequency of output wave. Design it for output frequency 2 KHZ and  $V_{O(PP)} = 7V$ . Supply voltage is 14 V.
- b) Explain the applications of Monostable Multivibrator.
- OR**
- Q.1** [12]
- a) Distinguish between signal generator and oscillator. In voltage controlled oscillator circuit if supply voltage is 12V,  $R_2 = 1.5K\Omega$ ,  $R_1=R_3 = 10 K\Omega$ ,  $C_1 = 0.001\mu F$ . Determine output frequency, Modulation in output frequency if Control voltage is varied between 9.5 and 11.5. Draw square waveform if modulating input is sine wave.
- b) Explain the operation of Astable Multivibrator with output waveforms. Determine frequency if  $R_A = 2.2 K\Omega$  ;  $R_B = 3.9 K\Omega$  and  $C = 0.1 \mu F$ .
- Q.2** [11]
- a) Design 2<sup>nd</sup> order low pass Butterworth filter at 1KHz cutoff frequency with pass band gain of 2. Plot its frequency response
- b) With the help of block diagram explain phase locked loop
- OR**
- Q.2** [11]
- a) Define demodulation. Describe DSB-SC system of communication with its advantages and disadvantages.
- b) Explain fixed voltage regulators and how it can be used to construct  $\pm 5 V$  fixed power supply
- Q.3** [12]
- Write short note on (Any three)
- a) High level AM transmitter
- b) Classification of filters with advantages of active filters.
- c) Switching regulators
- d) General block diagram of communication



## Section – II

Q.4

- a). Derive gain equation for Inverting amplifier configuration.
- b). Discuss types of integrated circuits and IC packaging.

OR

Q.4

- a). Explain Output characteristic of OP-AMP.
- b). Derive input and output resistance with feedback for Inverting amplifier configuration.

Q.5

- a).
  - a). Explain SCHMITT trigger.
  - b). Explain sample and hold circuit.
- b). Explain differentiator with neat figure and also derive its equation.

OR

Q.5

- a). Explain V to F converter and draw internal circuit.
- b). Explain peak detector and sample and hold circuit.

Q.6

- a). Draw and explain equivalent circuit of OPAMP.
- b). How to determine bandwidth of AC Amplifier.
- c). Design peaking amplifier for gain of 10 at 12kHz peak frequency. Assume necessary data.

-----END OF PAPER-----