

GANPAT UNIVERSITY

M.Tech Semester –II (EC) Regular Examination, April-June 2016

(3EC 205 –[1]) RF Circuits and Systems

Max. Time: 3 Hrs.]

[Max. Marks: 60

Instructions:

1. Attempt **all** questions.
2. Answers to the **two** sections must be written in **separate** answer books.
3. Figures to the **right** indicate full marks.
4. Assume suitable data, if necessary.

SECTION-I

- Q-1 (A) A silicon bipolar junction transistor has the following scattering parameters at GHz, 5
with a 50Ω reference impedance:
 $S_{11} = 0.38 \angle -158^\circ$,
 $S_{12} = 0.11 \angle 54^\circ$,
 $S_{21} = 3.50 \angle 80^\circ$,
 $S_{22} = 0.40 \angle -43^\circ$
 The source impedance is $Z_S = 25 \Omega$ and the load impedance is $Z_L = 40 \Omega$. Compute the power gain, the available power gain, and the transducer power gain.
- (B) What do you mean by Unconditional stability concept in amplifier design? Derive the 5
equation for the output stability circle for microwave amplifier design.
- OR**
- Q-1 (A) What do you mean by conditional stability concept in amplifier design? Derive required 5
equations for the input stability circle for microwave amplifier design.
- (B) What is Nyquist or Barkhausen criterion for oscillator functioning? Derive basic 5
equations for design of Colpitt oscillator based on CE configuration using general analysis method for it.
- Q-2 (A) Discuss in detail about Double balanced mixers. 5
(B) Write short note on Dielectric resonator oscillators. 5
- OR**
- Q-2 (A) Explain about working of single ended mixers with suitable diagrams. 5
(B) What is importance of phase noise in oscillator design? Discuss about it in detail. 5
- Q-3 (A) Write short notes on Microwave sensors. 3
(B) Draw basic block diagram of ROF based system and explain functionality of its each 3
block.
(C) Write short note on Microwave Radiometer. 4

SECTION - II

- Q-4 (A) With help of Planck's blackbody radiation law derive equation for power of thermal noise. What you will say about ultraviolet catastrophe condition with reference to it? 5
(B) Derive equation for Noise Figure and effective noise temperature of a three stage cascaded system. 5

OR

- Q-4 (A) Discuss in detail about Measurement of Noise Temperature (Y factor) method. 5
(B) Briefly discuss about tests for unconditional stability for amplifier design procedure. 5

- Q-5 (A) A receiver has a noise figure of 7 dB, a 1 dB compression point of 25 dBm (referenced to output), a gain of 40 dB, and a third-order intercept point of 35 dBm (referenced to output). If the receiver is fed with an antenna having a noise temperature of $T_A = 150^\circ \text{K}$, and the desired output SNR is 10 dB, find values of linear and spurious free dynamic ranges and give your comment form those values. Assume a receiver bandwidth of 100 MHz. 5
(B) Write short note on Single-pole PIN diode switches. 5

OR

- Q-5 (A) An X-band amplifier has a gain of 20 dB and a 1 GHz bandwidth. Its equivalent noise temperature is to be measured via the Y-factor method. The following data are obtained:
For $T_1 = 290 \text{ K}$, $N_1 = -62.0 \text{ dBm}$.
For $T_2 = 77 \text{ K}$, $N_2 = -64.7 \text{ dBm}$.
Determine the equivalent noise temperature of the amplifier. If the amplifier is used with a source having an equivalent noise temperature of $T_s = 450^\circ \text{K}$, what is the output noise power from the amplifier, in dBm? 5
(B) With required equations describe about low noise amplifier design issue. 5

- Q-6 (A) Explain concept of the Third-order intercept point for a nonlinear component working. 3
(B) Discuss briefly about Broadband high power and multistage Amplifiers. 3
(C) Derive required equation for Noise Figure of a Passive Two-Port Network. 4

END OF PAPER